

Chapter 1

Introduction

eThinking in Circuits with PSpice

Mechanical Engineering
National Central University

February 13, 2012 – February 11, 2022

Outlines

1 Electrical Components

- Quantities
- Relationships

2 Electrical Laws

- Ohm's law
- Faraday's law
- Henry's law

3 Electrical Sources

- Ideal independent sources
- Ideal dependent sources

Electrical Components

Passive() elements: resistor, capacitor, inductor, transformer

Active() elements: transistor, motor, generator.

- Charge(): $+q$ & $-q$, $\pm 1.602 \times 10^{-19}$ coulomb()

Electrical Components

Passive() elements: **resistor**, **capacitor**, **inductor**, transformer

Active() elements: **transistor**, motor, generator.

- Charge(): $+q$ & $-q$, $\pm 1.602 \times 10^{-19}$ coulomb()

- Current:

$$i = \frac{dq}{dt} = \frac{dq^+}{dt} + \frac{dq^-}{dt} \quad (A = \frac{C}{s}), \quad q(t) = \int_0^t i(\tau) d\tau + q(0)$$

$$\left. \begin{array}{l} \leftarrow \oplus(q_L^+) \quad \oplus(q_R^+) \rightarrow \\ \leftarrow \ominus(q_L^-) \quad \ominus(q_R^-) \rightarrow \end{array} \right\} \text{reference direction} \rightarrow i$$

$$q = q_R^+ - q_L^+ + (q_R^- - q_L^-)$$

Current Convention: Current has direction. AC & DC

Electrical Components

Passive() elements: resistor, capacitor, inductor, transformer

Active() elements: transistor, motor, generator.

- Charge(): $+q$ & $-q$, $\pm 1.602 \times 10^{-19}$ coulomb()

- Current:

$$i = \frac{dq}{dt} = \frac{dq^+}{dt} + \frac{dq^-}{dt} \quad (A = \frac{C}{s}), \quad q(t) = \int_0^t i(\tau) d\tau + q(0)$$

$$\left. \begin{array}{l} \leftarrow \oplus(q_L^+) \quad \oplus(q_R^+) \rightarrow \\ \leftarrow \ominus(q_L^-) \quad \ominus(q_R^-) \rightarrow \end{array} \right\} \text{reference direction} \rightarrow i$$

$$q = q_R^+ - q_L^+ + (q_R^- - q_L^-)$$


Current Convention: Current has direction. AC & DC

- Voltage: $v = \frac{d\omega}{dq}$ ($V = \frac{J}{C}$)



Voltage Convention: Voltage has polarity. + polarity has higher potential than - polarity. It DOES NOT mean + is of positive value and - is of negative value.

Continued

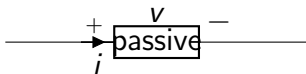

Passive elements: Current entering + consumes power.

- Energy and Power


$$dw = v \cdot dq = v \frac{dq}{dt} \cdot dt = \underline{v i dt}$$

$$w = \int_{t_1}^{t_2} v i dt = \int_{t_1}^{t_2} p dt$$

$$\underline{p = \frac{dw}{dt} = \frac{v dq}{dt} = v i} \quad (\text{volts} \times \text{amp} = \frac{J}{C} \times \frac{C}{s} = \frac{J}{s} = \text{Watts})$$

$$P_{av} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} v i dt = \underline{\text{Average power over } t_2 - t_1}.$$

Continued

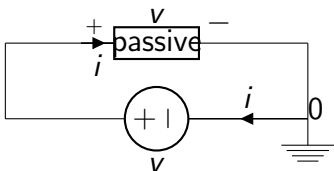

Passive elements: Current entering + consumes power.

Active element: Current leaving + generates power.

- Energy and Power


$$dw = v \cdot dq = v \frac{dq}{dt} \cdot dt = vidt$$

$$w = \int_{t_1}^{t_2} vidt = \int_{t_1}^{t_2} pdt$$

$$p = \frac{dw}{dt} = \frac{vdq}{dt} = vi \quad (\text{volts} \times \text{amp} = \frac{J}{C} \times \frac{C}{s} = \frac{J}{s} = \text{Watts})$$

$$P_{av} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} vi \, dt = \text{Average power over } t_2 - t_1.$$

Overall Closed-loop Circuit

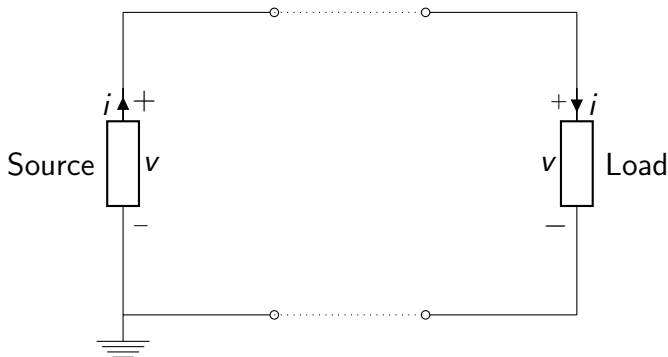

Passive reference configuration:


Sources: provide, deliver, send, generate

Loads: absorb, consume, receive, draw

Current has direction.

Voltage has polarities.

Overall Closed-loop Circuit

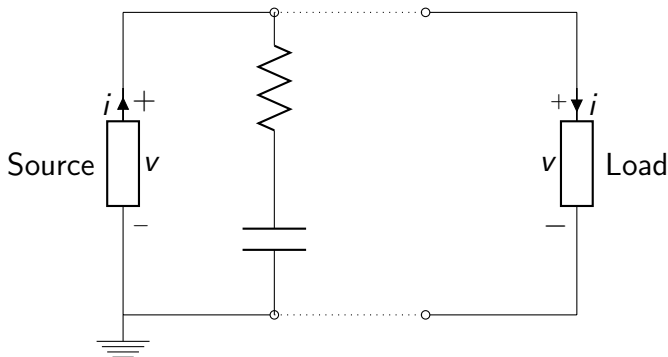

Passive reference configuration:


Sources: provide, deliver, send, generate

Loads: absorb, consume, receive, draw

Current has direction.

Voltage has polarities.

Overall Closed-loop Circuit

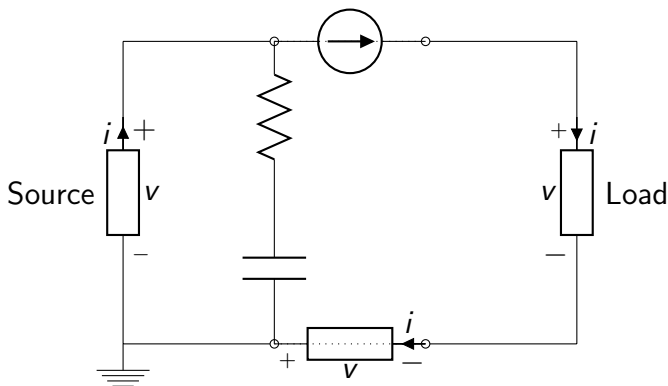

Passive reference configuration:


Sources: provide, deliver, send, generate

Loads: absorb, consume, receive, draw

Current has direction.

Voltage has polarities.

Overall Closed-loop Circuit

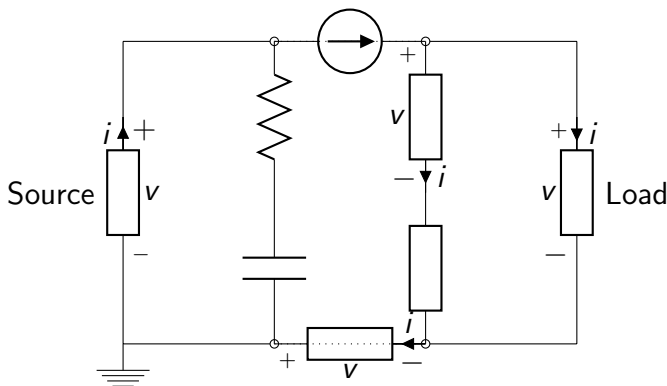

Passive reference configuration:

Sources: provide, deliver, send, generate


Loads: absorb, consume, receive, draw

Current has direction.

Voltage has polarities.



Overall Closed-loop Circuit

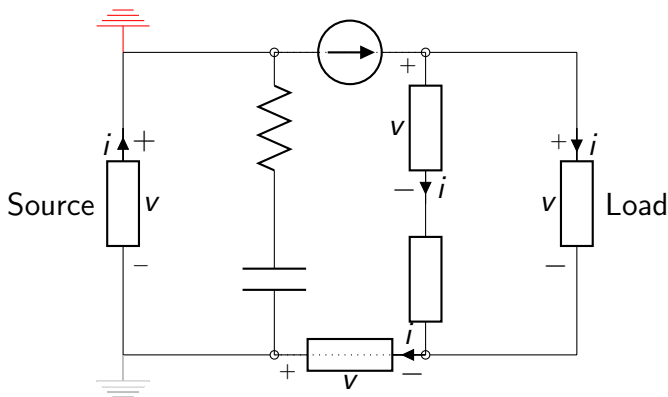

Passive reference configuration:


Sources: provide, deliver, send, generate

Loads: absorb, consume, receive, draw

Current has direction.

Voltage has polarities.

Resistors

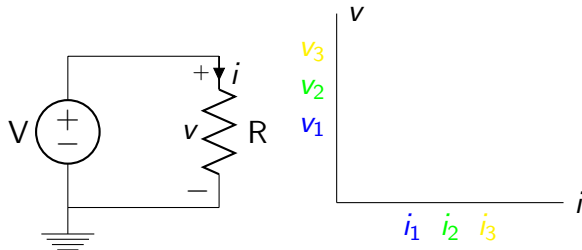


$$v = iR, \quad \text{Current entering +}$$

$$v = -iR, \quad \text{Current entering -}$$

$$p = vi = (iR)i = i^2 R = \frac{v^2}{R}$$

$$\omega = \int_{t_1}^{t_2} p dt = R \int_{t_1}^{t_2} i^2 dt = \frac{1}{R} \int_{t_1}^{t_2} v^2 dt$$

Resistors

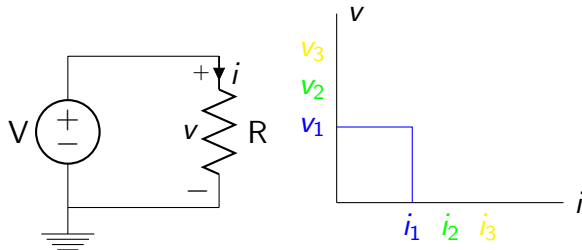


$v = iR$, Current entering +

$v = -iR$, Current entering -

$$\underline{p} = \underline{vi} = (iR)i = \underline{i^2 R} = \underline{\frac{v^2}{R}}$$

$$\omega = \int_{t_1}^{t_2} p dt = R \int_{t_1}^{t_2} \underline{i^2} dt = \underline{\frac{1}{R} \int_{t_1}^{t_2} v^2 dt}$$

Resistors

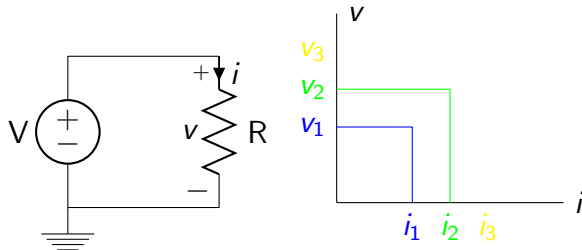


$$v = iR, \quad \text{Current entering +}$$

$$v = -iR, \quad \text{Current entering -}$$

$$p = vi = (iR)i = i^2R = \frac{v^2}{R}$$

$$\omega = \int_{t_1}^{t_2} p dt = R \int_{t_1}^{t_2} i^2 dt = \frac{1}{R} \int_{t_1}^{t_2} v^2 dt$$

Resistors

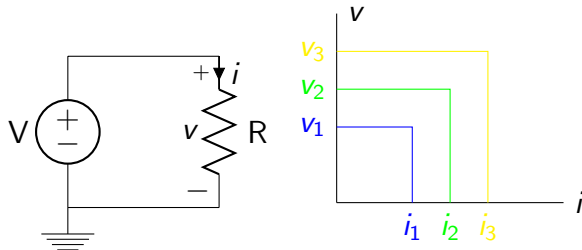



$$v = iR, \quad \text{Current entering +}$$

$$v = -iR, \quad \text{Current entering -}$$

$$p = vi = (iR)i = i^2R = \frac{v^2}{R}$$

$$\omega = \int_{t_1}^{t_2} p dt = R \int_{t_1}^{t_2} i^2 dt = \frac{1}{R} \int_{t_1}^{t_2} v^2 dt$$

Resistors

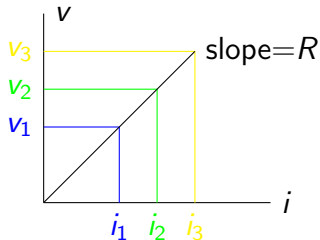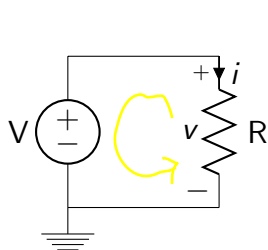

$$v = iR, \quad \text{Current entering +}$$


$$v = -iR, \quad \text{Current entering -}$$

$$i = \frac{V}{R}$$

$$p = \underline{vi} = (iR)i = i^2 R = \frac{v^2}{R}$$

$$\omega = \int_{t_1}^{t_2} p dt = R \int_{t_1}^{t_2} i^2 dt = \frac{1}{R} \int_{t_1}^{t_2} v^2 dt$$

Capacitors

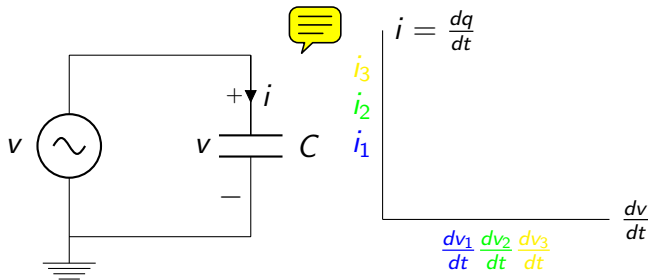


$$i = \frac{dq}{dt} = C \frac{dv}{dt}, \quad \text{Current entering +}$$

$$i = -C \frac{dv}{dt}, \quad \text{Current entering -}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$p = vi = v(C \frac{dv}{dt})$$

Capacitors

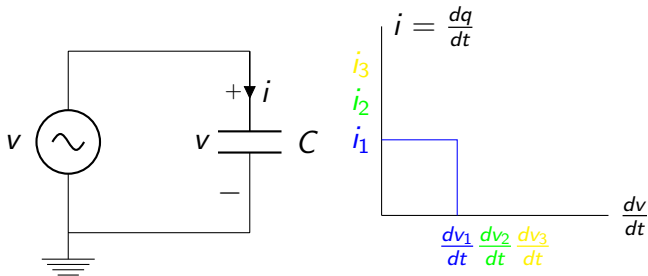


$$i = \frac{dq}{dt} = C \frac{dv}{dt}, \quad \text{Current entering +}$$

$$i = -C \frac{dv}{dt}, \quad \text{Current entering -}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$p = vi = v \left(C \frac{dv}{dt} \right)$$

Capacitors

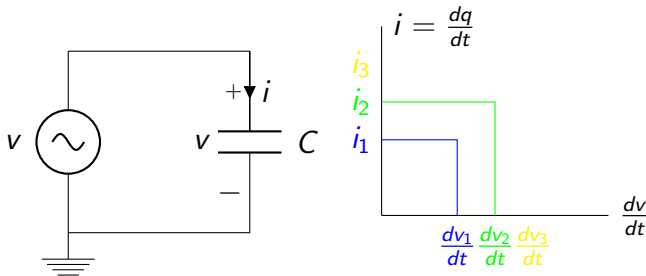


$$i = \frac{dq}{dt} = C \frac{dv}{dt}, \quad \text{Current entering +}$$

$$i = -C \frac{dv}{dt}, \quad \text{Current entering -}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$p = vi = v \left(C \frac{dv}{dt} \right)$$

Capacitors

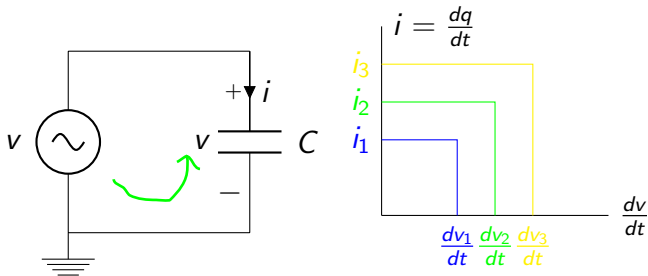



$$i = \frac{dq}{dt} = C \frac{dv}{dt}, \quad \text{Current entering +}$$

$$i = -C \frac{dv}{dt}, \quad \text{Current entering -}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$p = vi = v \left(C \frac{dv}{dt} \right)$$

Capacitors

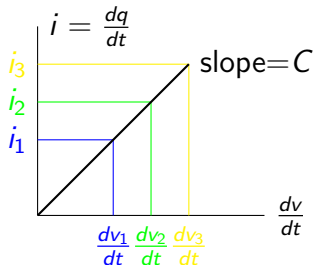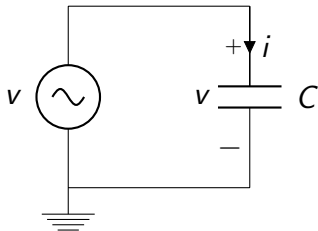


$$i = \frac{dq}{dt} = C \frac{dv}{dt}, \quad \text{Current entering +}$$

$$i = -C \frac{dv}{dt}, \quad \text{Current entering -}$$


$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$p = vi = v(C \frac{dv}{dt})$$

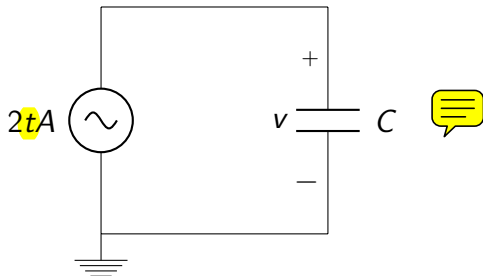

Here, we assume $C = 1$ and $i(t) = 2t$, thus $v(t) = t^2$.

Inductors

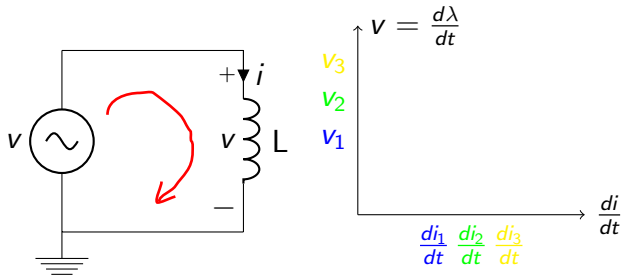

$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}, \quad \text{Current entering } +$$


$$v = \ominus L \frac{di}{dt}, \quad \text{Current entering } -$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$p(t) = vi = \left(L \frac{di}{dt}\right) i$$

$$w(t) = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau = \frac{1}{2} L i^2(t) = \frac{\lambda^2(t)}{2L}$$

Inductors

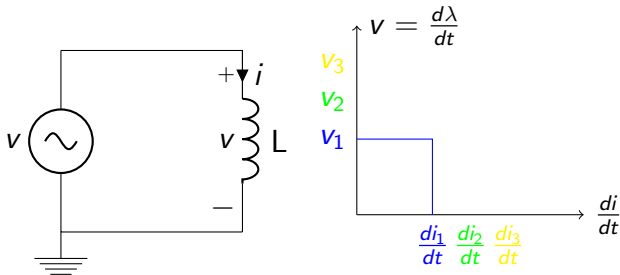

$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}, \quad \text{Current entering +}$$


$$v = -L \frac{di}{dt}, \quad \text{Current entering -}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$p(t) = vi = \left(L \frac{di}{dt}\right) i$$

$$w(t) = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau = \frac{1}{2} Li^2(t) = \frac{\lambda^2(t)}{2L}$$

Inductors

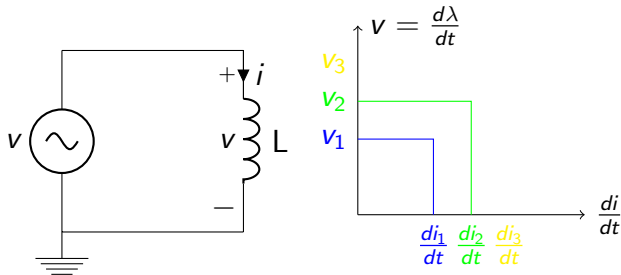

$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}, \quad \text{Current entering +}$$


$$v = -L \frac{di}{dt}, \quad \text{Current entering -}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$p(t) = vi = \left(L \frac{di}{dt}\right) i$$

$$w(t) = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau = \frac{1}{2} L i^2(t) = \frac{\lambda^2(t)}{2L}$$

Inductors

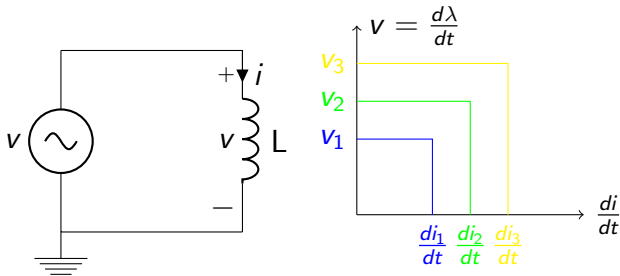

$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}, \quad \text{Current entering +}$$



$$v = -L \frac{di}{dt}, \quad \text{Current entering -}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$p(t) = vi = \left(L \frac{di}{dt}\right) i$$

$$w(t) = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau = \frac{1}{2} L i^2(t) = \frac{\lambda^2(t)}{2L}$$

Inductors

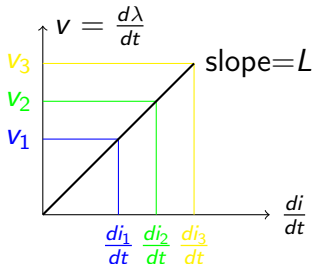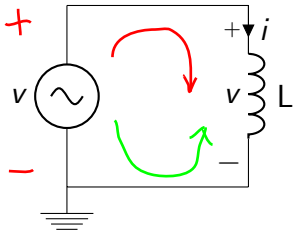

$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}, \quad \text{Current entering } +$$



$$v = -L \frac{di}{dt}, \quad \text{Current entering } -$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v(\tau) d\tau + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = \underline{i(t_0)} + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$p(t) = \underline{vi} = \left(L \frac{di}{dt}\right) i$$


$$w(t) = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau = \underline{\frac{1}{2} Li^2(t)} = \frac{\lambda^2(t)}{2L}$$

Ideal independent VOLTAGE source

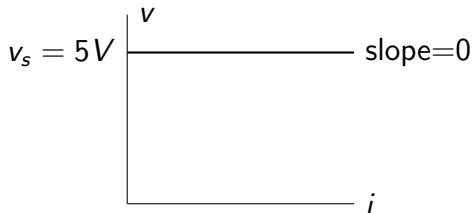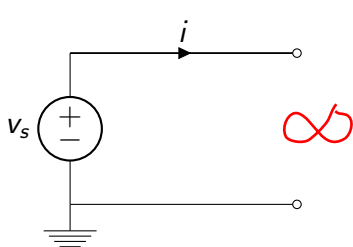


Regardless of the load, the source ALWAYS provides fixed voltage V_s , thus load is always fixed too due to the parallel structure. But the current i provided by voltage source will change.

Ideal independent VOLTAGE source


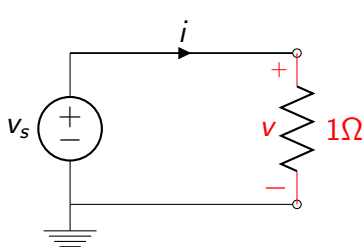


$$i = \frac{5}{1} = 5A,$$

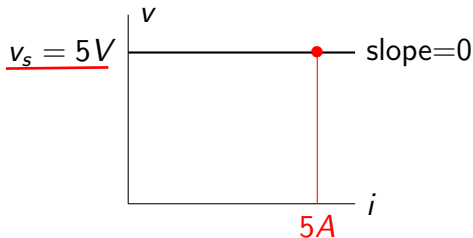

Regardless of the load, the source ALWAYS provides fixed voltage V_s , thus load is always fixed too due to the parallel structure. But the current i provided by voltage source will change.



Ideal independent VOLTAGE source

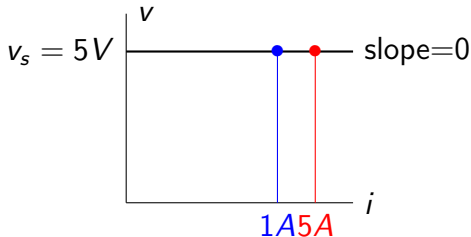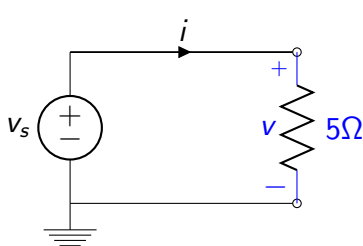

$$i = \frac{5}{1} = 5A, \quad i = \frac{5}{5} = 1A,$$

Regardless of the load, the source ALWAYS provides fixed voltage V_s , thus load is always fixed too due to the parallel structure. But the current i provided by voltage source will change.



Ideal independent VOLTAGE source

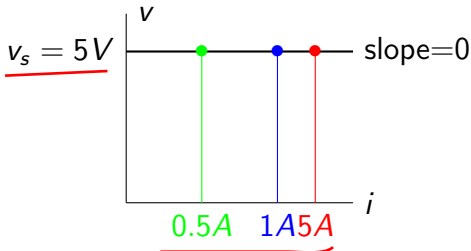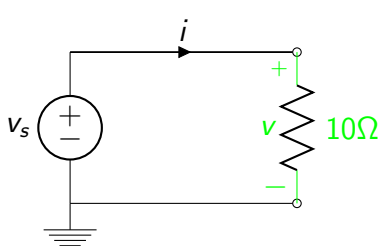

$$i = \frac{5}{1} = 5A, \quad i = \frac{5}{5} = 1A, \quad i = \frac{5}{10} = 0.5A$$

Regardless of the load, the source **ALWAYS** provides fixed voltage V_s , thus load is always fixed too due to the parallel structure. But the **current i** provided by voltage source **will change**.

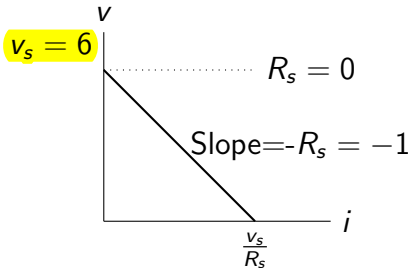
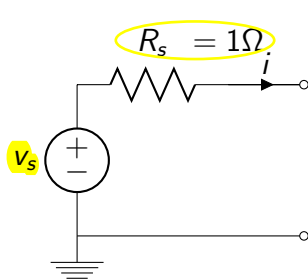
Ideal independent VOLTAGE source **with** internal resistor



With internal resistor, the output/load voltage and current will change, but the source remains fixed at V_s .

Voltage source in series with a resistor.

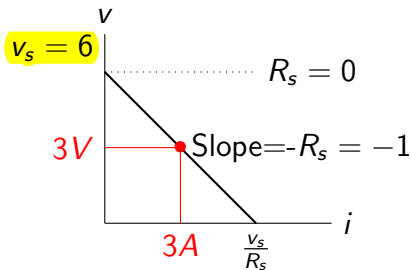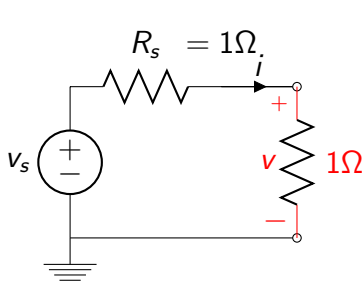Ideal independent VOLTAGE source with internal resistor





$$i = \frac{6}{2} = 3A,$$

With internal resistor, the output/load voltage and current will change, but the source remains fixed at V_s .

Voltage source in series with a resistor.

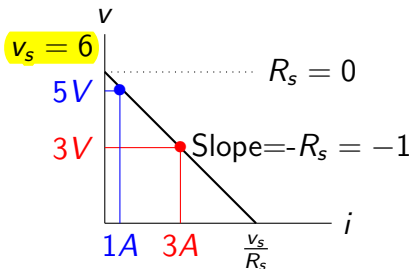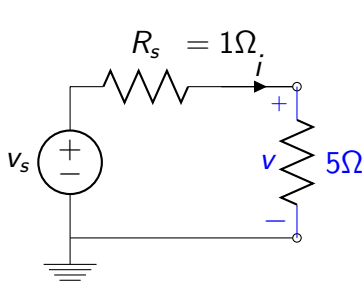Ideal independent VOLTAGE source with internal resistor





$$i = \frac{6}{2} = 3A, \quad i = \frac{6}{6} = 1A,$$

With internal resistor, the output/load voltage and current will change, but the source remains fixed at V_s .


Voltage source in series with a resistor.

Ideal independent CURRENT source

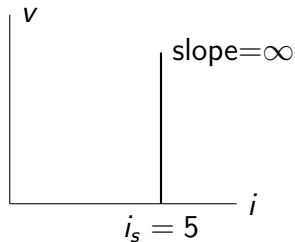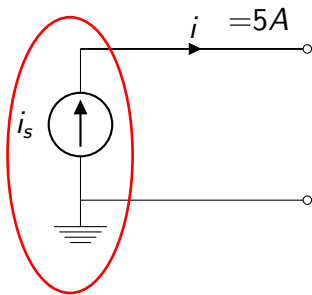


Regardless of loads, the current ALWAYS provides a fixed current I_s . The output current i is fixed too due to series structure. But the output/load voltage v changes accordingly due to parallel structure.

Ideal independent CURRENT source

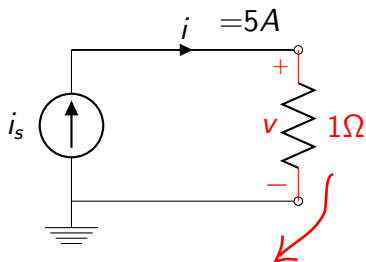


$$v = 5 \times 1 = 5V,$$

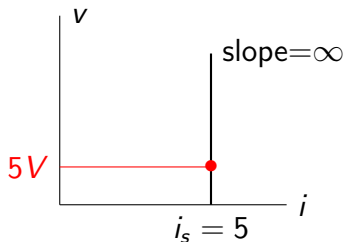


Regardless of loads, the current ALWAYS provides a fixed current I_s . The output current i is fixed too due to series structure. But the output/load voltage v changes accordingly due to parallel structure.

Ideal independent CURRENT source

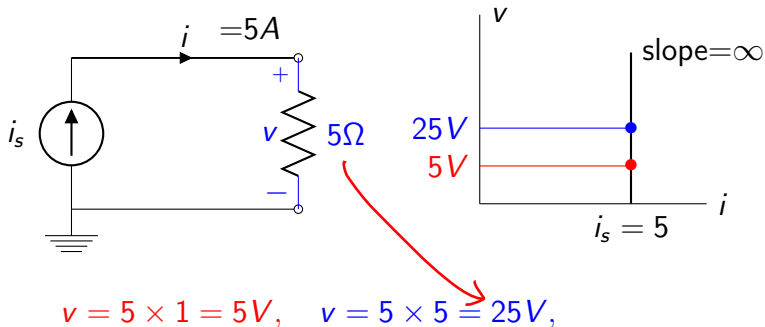

Regardless of loads, the current ALWAYS provides a fixed current I_s . The output current i is fixed too due to series structure. But the output/load voltage v changes accordingly due to parallel structure.



Ideal independent CURRENT source

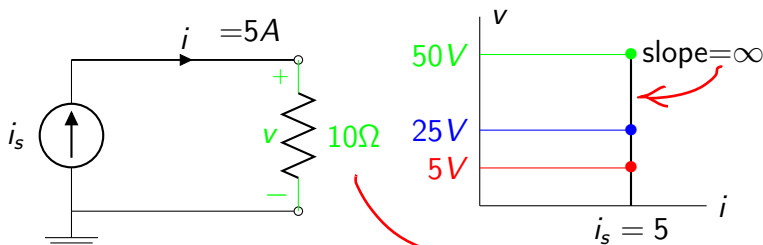

$$v = 5 \times 1 = 5V, \quad v = 5 \times 5 = 25V, \quad v = 5 \times 10 = 50V$$

Regardless of loads, the current **ALWAYS** provides a **fixed current i_s** .
 The output current i is fixed too due to series structure. But the output/load voltage v changes accordingly due to parallel structure.

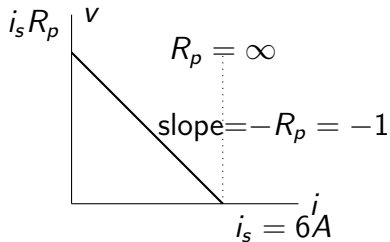
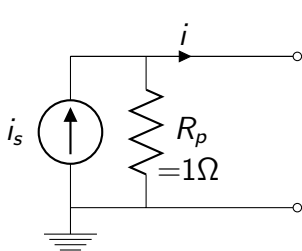
Ideal independent CURRENT source with internal resistor



With internal resistor, the output/load voltage and current will change, but the source remains fixed at i_s .

Current source in parallel with a resistor.

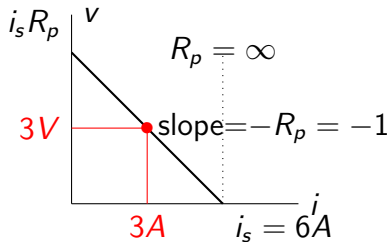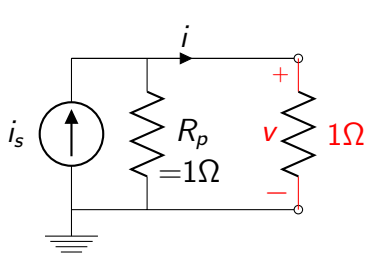Ideal independent CURRENT source with internal resistor





$$v = 3 \times 1 = 3V$$

With internal resistor, the output/load voltage and current will change, but the source remains fixed at i_s .

Current source in parallel with a resistor.

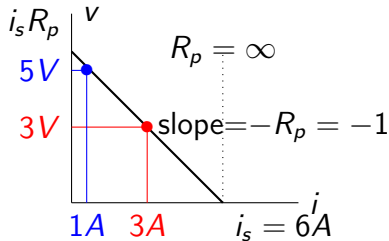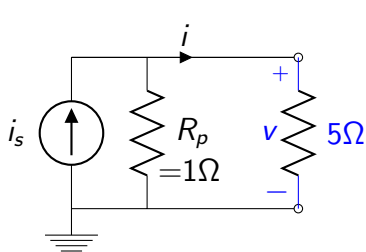Ideal independent CURRENT source with internal resistor




$$v = 3 \times 1 = 3V \quad v = \frac{1 \times 6}{6} \times 5 = 5V$$

With internal resistor, the output/load voltage and current will change, but the source remains fixed at i_s .



Current source in parallel with a resistor.

Voltage-controlled

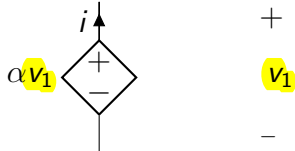Voltage-Controlled Voltage Source (VCVS):



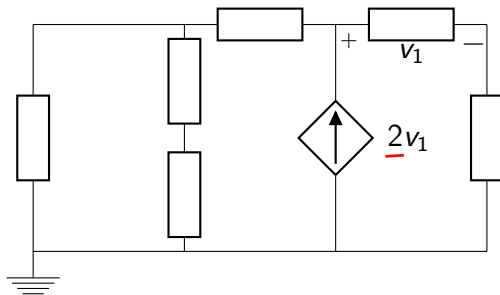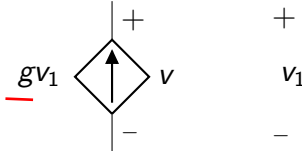
Voltage-Controlled Current Source (VCCS):





A circuit example

Current-controlled

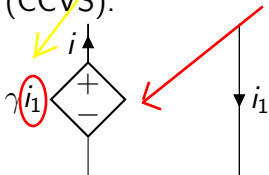Current-Controlled Voltage Source (CCVS):



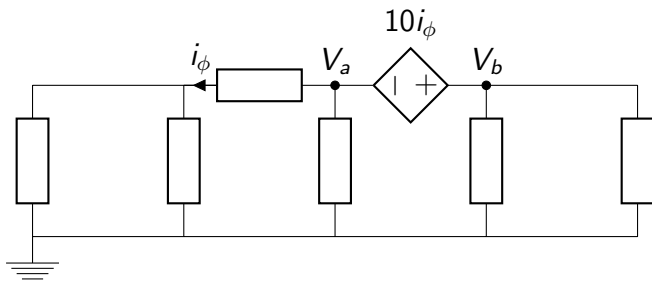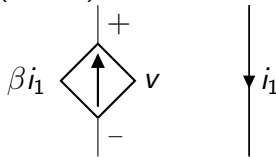Current-Controlled Current Source (CCCS):



A circuit example