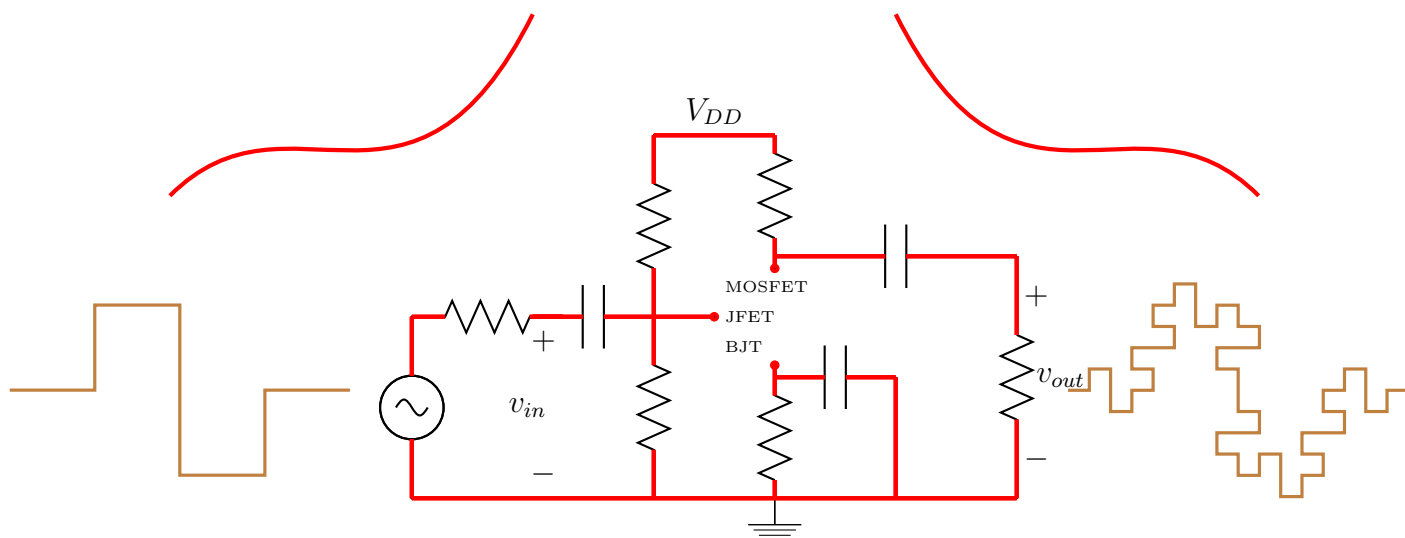



eThinking

in Circuits


with PSpice®



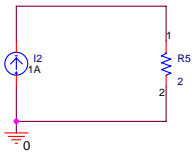- 1 Introduction
- 2 Circuit Laws
- 3 DC Circuits
- 4 AC Circuits
- 5 Transient Responses
- 6 Frequency Responses
- 7 Diodes
- 8 Operational Amplifiers
- 9 Bipolar Transistors
- 10 Unipolar Transistors
- 11 PSpice Simulation Results




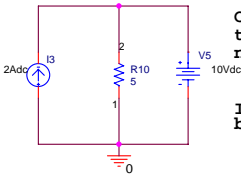1. Construct the circuit on the left.
2. To verify Ohms' Law, open up the Simulation Settings and check DC Sweep/Primary Sweep, fill in the variable name I2, then Start value 0, End value 10, and increment 2 using linear scale.
3. Run the simulation by clicking the Big Blue Right Arrow.
4. When the probe window shows up, click Trace/Add Trace to find V1(R5) for output.
5. To find the numerical value of a particular point, click Trace/Cursor to get the cursor, move the cursor to the point you want, and click Plot/Label/Mark to add the numerical value on the graph.




Or simply choose DC Bias Point analysis by editing Simulation Settings again. Then run the simulation. After that, click V and/or I to obtain the answer right away. But notice that this is valid only for one-time solution.

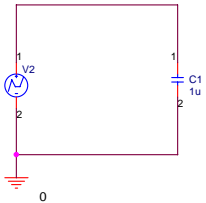In the second example, there are two independent sources. You may explore the solution by using DC analysis again.



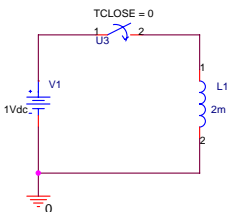1. Construct the circuit on the left.
2. To verify Faradays' Law, open up the Simulation Settings and select Time Domain Transient analysis, set time period to 0.01ms.
3. Run the simulation.
4. When Probe window pops up, click Trace/Add Trace to select V1(V2) and I(C1), using comma to separate them.

You may use the circuit above with C being replaced by L and voltage source replaced by IPWL, then verify the Henry's Law $v=L \, di/dt$. Or equivalently, check its integral form as shown in the last circuit.




1. Construct the circuit on the left.
2. Open up the Simulation Settings, click Time Domain Transient and fill in Tstop=40ms.
3. Click the Blue Arrow.
4. When the Probe Window shows up, click Trace/Add Trace to add I(L1) and see the result.


Title		
Electrical Laws		
Size	Document Number	Rev
A4	Chapter 1, JCLO	1
Date:	Wednesday, August 24, 2011	Sheet 1 of 1

To solve DC circuits for current and voltage is to


1. Open up the Simulation Settings and select Bias Point analysis.
2. Run the simulation by clicking the Big Blue Arrow.
3. Once it is done, click V, I, W icons respectively to find solutions printed on the circuits.

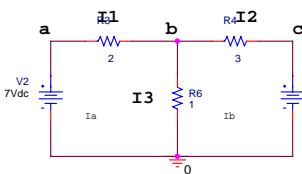


Example 2.5-2.7

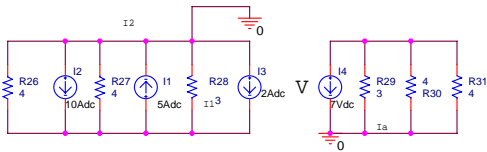


Example 2.13

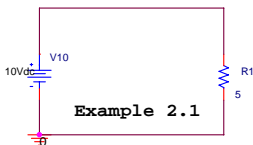

Example 2.1


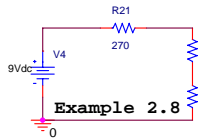


Example 2.8

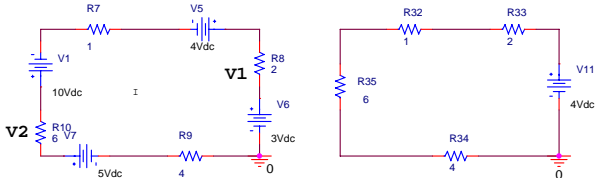


Example 2.10

Example 2.3

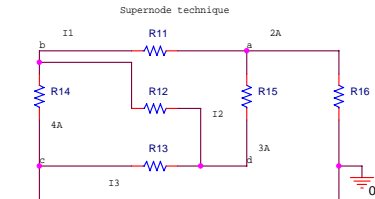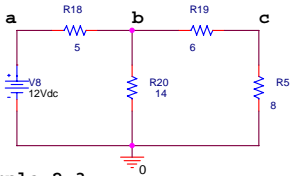

Example 2.4

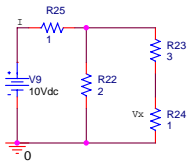


Example 2.12


File		
Circuit Laws		
Size	Document Number	Rev
A4	Chapter 2, Page 1, JCLO	1
Date:	Wednesday, August 24, 2011	Sheet 1 of 1

v-i Characteristics for Thevenin equivalent


- 1. Construct the circuits below.
- 2. Open up the Simulation Settings, check the Time Domain Transient analysis, and set time period to 10ms.
- 3. Run the simulation. (it is noted that the switch yields short- and open-circuits)
- 4. Click Trace/Add Trace to select I(U?:2).for y-axis.
- 5. Since time domain t is the default x-axis, we need to change it. Click Plot/Axis Setting/Axis Variables to select x axis = V(U?:2). The slope is 1/R.
- 6. If one exahcnges x and y axis, then the slope is R.

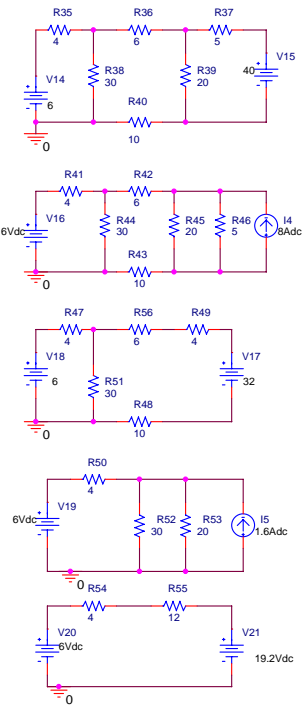

Example 3.2

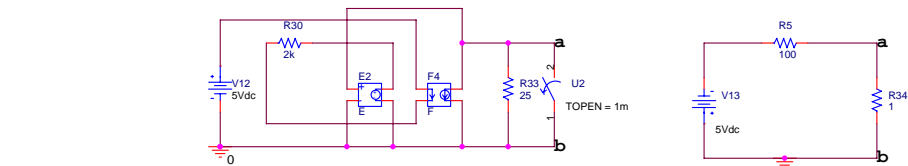

Examples 3.5

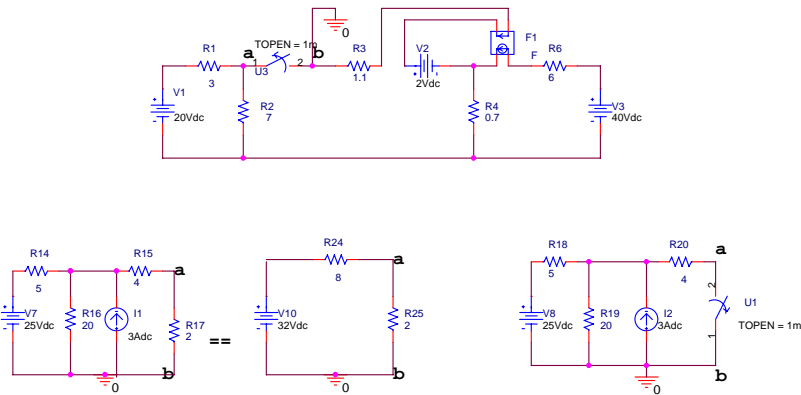


Examples 3.3-3.4

Title		
DC Circuit Analysis, Equivalence and Thevenin		
Size	Document Number	Rev
A4	Chapter 3, Page 1, JCLO	1
Date:	Wednesday, August 24, 2011	Sheet 1 of 4


Loop-Current Approach

To find solutions for the the problems below is straightforward.


- 1. Open up Simulation Settings and choose Bias Point analysis.
- 2. Click the Big Blue Arrow to Run.
- 3. After simulation is complete, click V and I icon at the top of Capture menu.

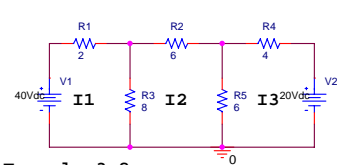


Example 3.8

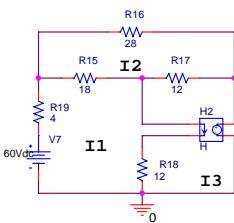


Example 3.11

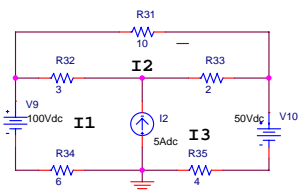


Example 3.14

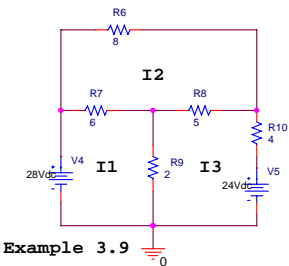


Example 3.9

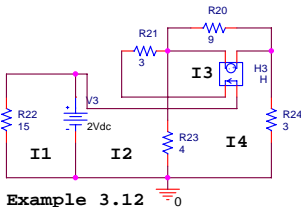

Example 3.12

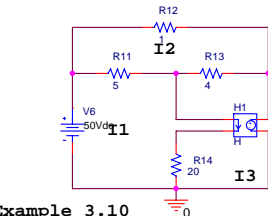

Example 3.10






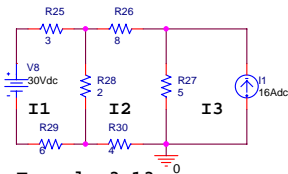


Example 3.13

Title		
DC Circuit Analysis		
Size	Document Number	Rev
A4	Chapter 3, Page 2, JCLO	
Date:	Wednesday, August 24, 2011	Sheet 2 of 4

Node-Voltage Approach

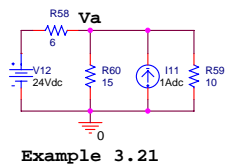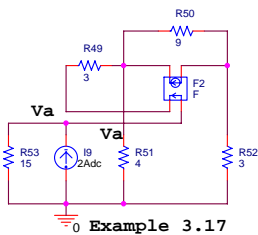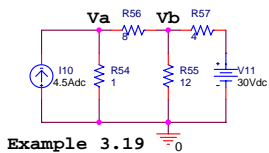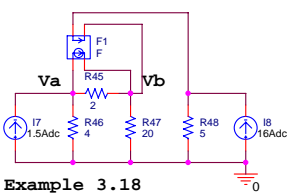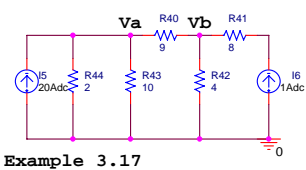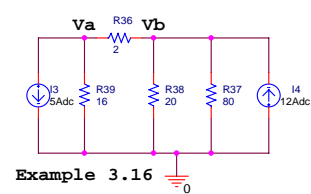- To find solutions for the the problems below is straightforward.
1. Open up the Simulation Settings and choose Bias Point analysis.
 2. Click the Big Blue Arrow to Run.
 3. After simulation is complete, click V and I icon at the top of Capture menu.



Title		
Circuit Analysis		
Size	Document Number	Rev
A4	Chapter 3, Page 3, JCLO	1
Date:	Tuesday, November 08, 2011	Sheet 3 of 4


Node-Voltage Approach

To find solutions for the the problems below is straightforward.


1. Open up Simulation Settings and choose Bias Point analysis.
2. Click Run.
3. After simulation is complete, click V and I icon at the top of Capture menu.

For supersition techniques


1. Basically this uses Bias Point analysis.
2. Replace on current source by an open circuit and replace an voltage source by an short circuit and leave only one active source to run.
3. Leave dependent sources alone.

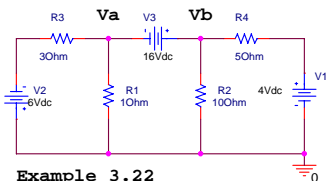


Example 3.22

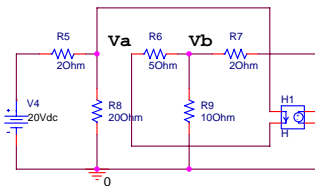


Example 3.23

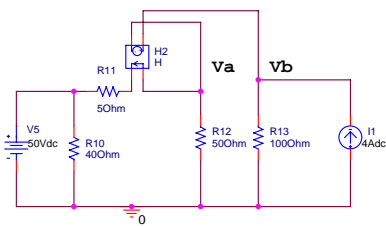

Example 3.24


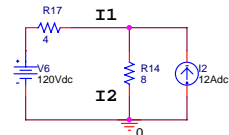


Example 3.26

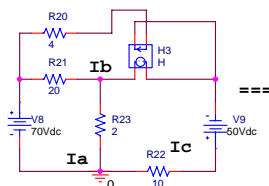


Example 3.27


Superposition

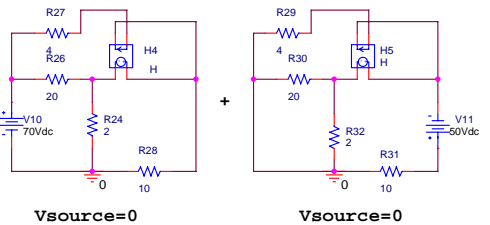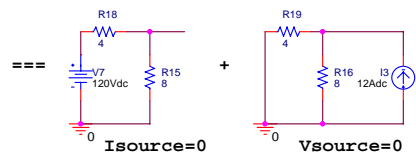


Title DC Circuit Analysis		
Size A4	Document Number Chapter 3, Page 4, JCLO	Rev 1
Date: Wednesday, August 24, 2011	Sheet 4	of 4

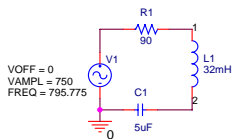

Example 4.3

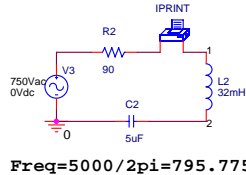

Freq=5000/2pi=795.775

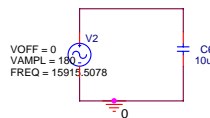


AC Power


$$\text{Real } P = v_i = 180 \times 180 \text{m} / 2 = 16.2 \text{W}$$

$$\text{Reactive } P = v_i = 180 \times 180 \times \cos(-90/57.3) / 2 = 0 \text{Var}$$


$$180 \cos(10^5 t), R = 1 \text{k}, C = 10 \text{u}, L = 10 \text{u}$$

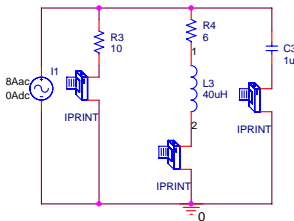

Example 4.4
Freq=200000/2pi=31831.015

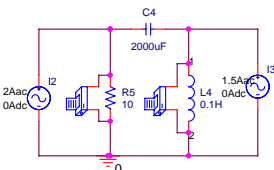

Example 4.5
Freq=100/2pi=15.915

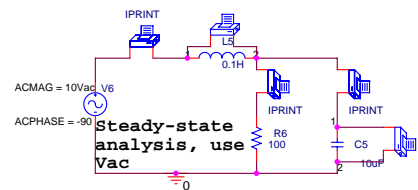


Steady-state analysis, use Vac

1. To find transient response selects Vsin/Isin functions as sources.
2. draw the circuit.
3. Open up the Simulation Settings to select Time Domain Transient and fill in the time period.
4. Run the simulation.
5. When probe window appears, click Trace/Add Trace to add desired variables for plottings.
5. Actually, the steady-state magnitude still can be found from the time trajectory.

1. To find steady-state response needs Vac/Iac functions
2. Select Simulation Settings/AC Sweep analysis and let Start = End frequency, using frequency in Hz, $w = 2\pi f$, NOT in w .
3. Click PSpice/Markers/Advanced and select appropriate markers, connect them to the node.
4. Run the simulation.
5. Results will be shown on the probe window.
6. Another way is to place VPRINT2 and IPRINT in circuits and the outputs are saved in the output text file.


Title		
Steady-State Analysis		
Size	Document Number	Rev
A4	Chapter4, Page 1	1
Date:	Monday, October 31, 2011	Sheet 1 of 1

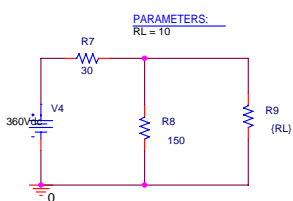


Maximum Power Transfer

1. Construct the circuit on the left.
2. Click R9 and fill in the value with {RL} (curly bracket is necessary)
3. Click Place Part/Special/PARAM and drag it to the place near R9.
4. Click the PARAMETERS to edit its property by adding a new column RL, insert a value except zero.
4. Click DC Sweep, check Global Parameter and give it a name RL, fill in (0:1:100) for sweeping range.
5. After Probe Window shows up, click Trace/Add Trace, select W(R9), to see the output vurve.

Title		
Transient		
Size	Document Number	Rev
A4	Chapter 4, Page 2	1
Date:	Tuesday, November 08, 2011	Sheet 1 of 1


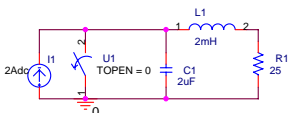


Example 5.1

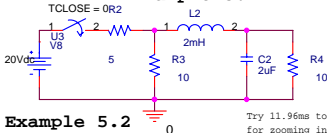


Example 5.2


Try 11.96ms to 12.06ms
for zooming in.

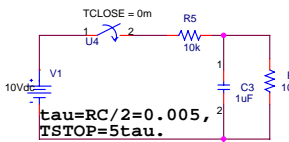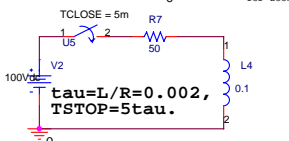

Example 5.3

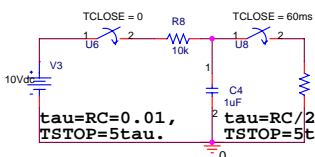

Example 5.4

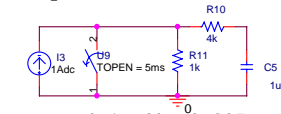


$\tau = (R1+R2)C = 0.005$,
 $TSTOP = 5\tau$.

Example 5.5

Transient simulation

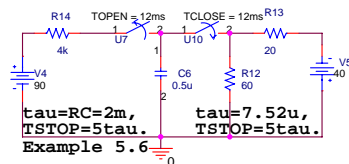
1. Open up Simulation Settings and choose Time Domain Transient analysis.
2. Fill in the Stop time. (Some suggestions are given)
3. Click Run.
4. Click Trace/Add Trace to select the variables of concern.
5. Check if the time trajectory is what you expect.



$\tau = RC = 2m$,
 $TSTOP = 5\tau$.


$\tau = 7.52u$,
 $TSTOP = 5\tau$.

Example 5.6

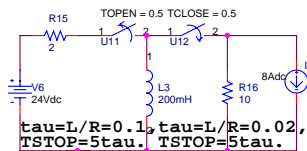


$\tau = L/R = 0.1$, $\tau = L/R = 0.02$,
 $TSTOP = 5\tau$, $TSTOP = 5\tau$.

Example 5.7

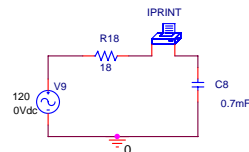


Steady-state
selects Vac
& AC sweep

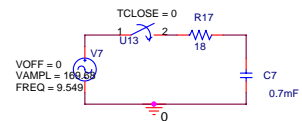


$\tau = RC = 0.0126$, $TSTOP = 5\tau$. Noting cos
should be changed to sin, adding 90
in phase.

Example 5.8


File		
Transient Analysis		
Size	Document Number	Rev
A4	Chapter 5, Page 1	1
Date:	Monday, October 31, 2011	Sheet 1 of 1

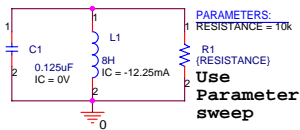


Examples 5.11-5.12

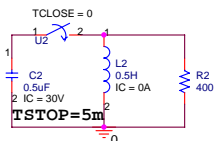

Example 5.13

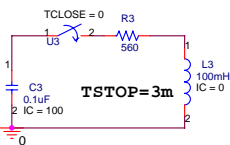


Example 5.14

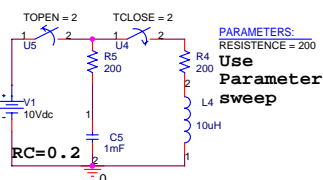


Example 5.15


TSTOP=10. Also try 10uH for inductor whose charateristic equation is $10^{-5}s^2 + 400s + 1000$

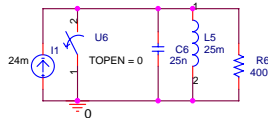

Example 5.16

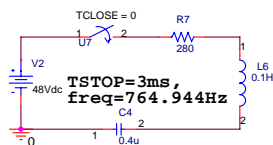

Example 5.17

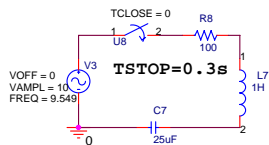

Example 5.19


Tranisent simulation

1. Open up Simulation Settings and choose Time Domain Transient analysis.
2. Fill in the Stop time.
3. Click Run.
4. When Probe Window appears, click Trace/Add Trace to add variables of concerns to see the plot.

Parameter Sweep


1. Open up Simulation Settings and select Time Domain Transient/Parameter Sweep.
2. Fill in Parameter Name xxx. and select a Sweep type or key in a few values of interests in the List.
3. Go back to your circuit and click the element to name its value to be {xxx}
4. Click Run.
5. See the results.

Title		
Switching Circuits		
Size	Document Number	Rev
A4	Chapter 5, Page2	1
Date:	Monday, October 31, 2011	Sheet 1 of 1

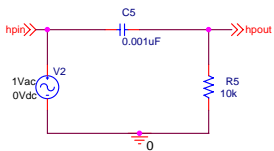

Example 6.2 -- Use VAC for frequency sweep

1. Construct the circuit on the left.
2. Click Simulation Settings, select Frequency Sweep, fill in (10:10:10E6).
3. When Probe Window appears, click Trace/Add Trace to add V(hpout) for linear scale or DB(V(hpout)) for log scale to generate the results.

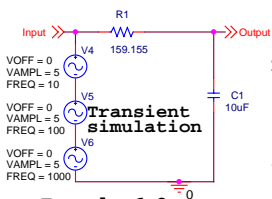


Example 6.3

Example 6.3

1. Construct the circuit on the left.
2. Open up Simulation Settings, select Time Domain Transient, fill in Stop time=100ms.
3. Run the Simulation.
4. When the Probe Window appears, click Trace/Add Trace to add V(output) and V(input) to see results, respectively.

For Bode Plot


1. Use VAC source.
2. Open up Simulation Settings, select AC Sweep and fill in frequency range (0.1:10:10E4).
3. When Probe Window appears, click Trace/Add Trace to add DB(V1(C2)) for log scale.

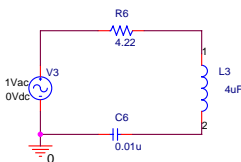

Example 6.4


1. Construct the circuit on the left.
 2. Open up Simulation Settings, click AC Sweep, fill in (1K:10 10E6) and check log scale.
 3. Run the Simulations.
 4. When the Prob Windeow appears, click Trace/Add Trace to add DB(I(L3))
- Freq=796159Hz<=>5002410rad/sec=w

Title		
Frequency Analysis		
Size	Document Number	Rev
A4	Chapter 6, Page 1	1
Date:	Monday, October 31, 2011	Sheet 1 of 1

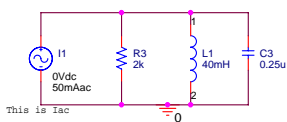


Example 6.6 -- Use IAC for frequency sweep

1. Construct the circuit on the left.
2. Click Simulation Settings, select Frequency Sweep, fill in (100:10:100K).
3. When Probe Window appears, click Trace/Add Trace to add I(R3) for linear scale or DB(I(R3)) for log scale to generate the results.

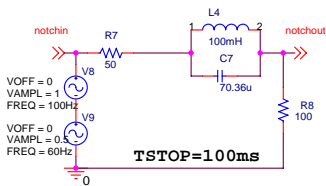


Example 6.7 Notch Filter

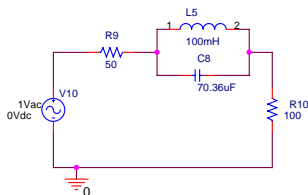1. Construct the circuit on the left.
2. Open up Simulation Settings, select Time Domain Transient, fill in Stop time=100ms.
3. Run the Simulation.
4. When the Probe Window appears, click Trace/Add Trace to add V(notchout) and V(notchin)-V9 to see results, respectively.



For Bode Plot


1. Use VAC source.
2. Open up Simulation Settings, select AC Sweep and fill in frequency range (10:10:100).
3. When Probe Window appears, click Trace/Add Trace to add DB(V1(R10)) for log scale.

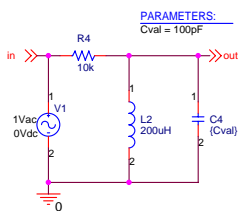


Example 6.9

1. Construct the circuit on the left.
2. Click C4 and fill in the value with {Cval} (the curly bracket is necessary)
3. Click Place Part/Special/PARAM and drag it to the place near C4.
4. Click the PARAMETERS to edit its property by adding a new column Cval, insert a value except zero.
5. Click dual AC Sweep, set (300K:10:3M) for primary, check Global Parameter and give it a name Cval, key in (100p, 200p, 300p) for Value list.
6. After Probe Window shows up, click Trace/Add Trace, select V(out), to see the output curve.


Title		
Frequency Analysis		
Size	Document Number	Rev
A4	Chapter 6, Page 2	1
Date	Tuesday, November 08, 2011	Sheet 1 of 1

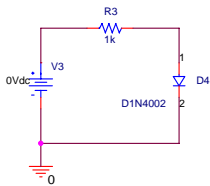

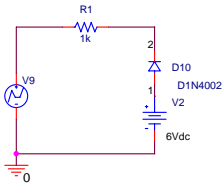1. Construct the circuit diagram on the left.
2. Open up the Simulation Settings by selecting DC Sweep where a dialog box will show up. Fill in sweep variable name V3 and sweep type (linear, start value -10, end value 2 and increments 0.1)
3. Run the simulation by clicking the blue solid right arrow.
4. After a blank graphic probe window appears, click Trace\Add Trace to add trace I(D4) for y-axis. Since the x-axis should be V(D4), we click Plot\Axis Settings to open up a dialog box and click axis variables to find V(D4:1).



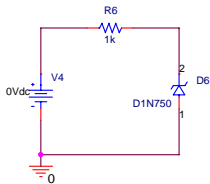
1. Construct the circuit on the left.
2. Use Transient analysis. Set final time to 10ms.
3. Run the simulation by clicking the big right arrow on the menu.
4. Click Trace\Add Trace to add input and output signals, V1(V9) and V2(D10)), respectively.
5. To find the transfer function, change x-axis in time to V1(V9).




1. Construct the circuit diagram on the left.
2. Edit simulation settings by selecting DC sweep where a dialog box will show up. Fill in Sweep Variable name V4 and Sweep Type (linear, start value 0, end value 20 and increments 0.1)
3. Run the simulation by clicking the blue solid right arrow.
4. After a blank graphic probe window appears, click Trace\Add Trace to add trace -I(D6) for y-axis. Since the x-axis should be V(D6), we click Plot\Axis Settings to open up a dialog box and click axis variables to find V(D6:2).
5. Draw a load line by clicking Plot\Label\Line and then draw the line from y-axis to x-axis or vice versa.

Title		
Diodes		
Size	Document Number	Rev
A4	Chapter 7, Page 1, JCLO	1
Date:	Tuesday, November 08, 2011	Sheet 1 of 2

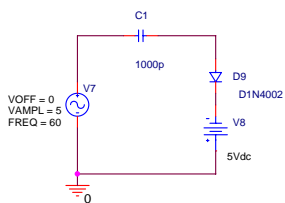
6. Find cursor from Trace\Cursur and click the intersection Q-point. Once this is done, go back to Plot\Label\Mark to insert the numerical value of the load line.



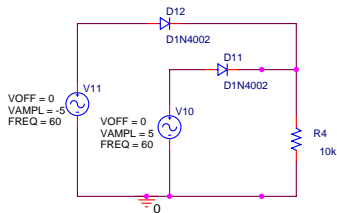1. Construct the circuit on the left.
2. Use Transient analysis. Set final time to 33.33m.
3. Run the simulation by clicking the big right arrow on the menu.
4. Click Trace\Add Trace to add input and output signals, V1(V7) and V1(D9), respectively.





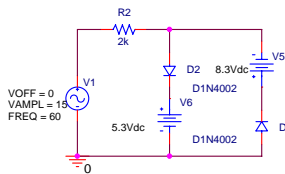1. Construct the circuit on the left.
2. Use Transient analysis. Set final time to 33.33m.
3. Run the simulation by clicking the big right arrow on the menu.
4. Click Trace\Add Trace to add input and output signals, V1(R4).
5. Add one smoothing capacitor in parallel with the load.




1. Use Transient analysis. Set final time to 33.33m.
2. Run simulation by clicking the big right arrow on the menu bar.
3. Click Trace/Add Trace to find V1(V1) and V1(D2)+V1(V6) respectively.
4. To find the transfer function V_{out}/V_{in} , click Plot/Add Plot to Window to generate a new blank plot and then Plot/Plot Settings/Axis Variables V1(V1) as x-axis and Add/Add Trace V1(D2)+V1(V6) as y axis.


Title		
Diodes		
Size	Document Number	Rev
A4	Chapter 7, Page 2, JCLO	<Rev Co
Date:	Monday, October 31, 2011	Sheet 2 of 2

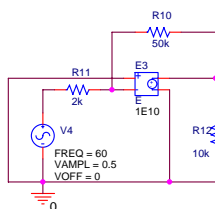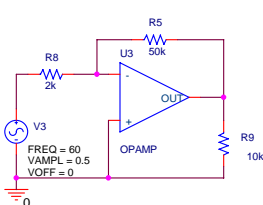

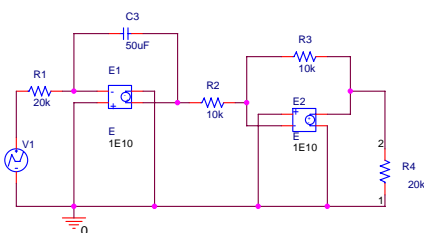1. Construct the circuit on the left.
2. Open up the Simulation Settings and select the Transient analysis, setting simulation time period to 33.33ms.
3. Run the simulation.
4. Click Trace/Add Trace to add V1(R9) and V1(R12) to see identical plot, meaning VCVS = op-amp.
5. Click Trace/Cursor/Displace to find cursor and then click Plot/Label/mark to insert numerical values.



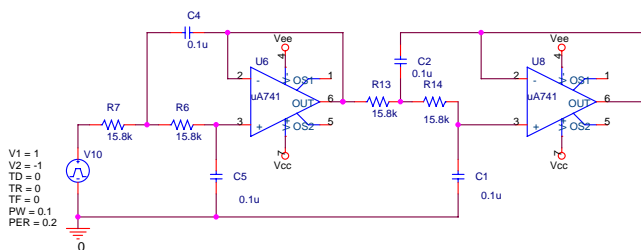
1. Construct the circuit on the left.
2. To verify integration, open up the Simulation Settings and select Time Domain Transient analysis, set time period to 4s. where pulse function of 4 second is given by VPWL.
3. Run the simulation.
4. When Probe window pops up, click Trace/Add Trace to select V1(V1) and V2(R2), using comma to separate them.




- To obtain Frequency response, use VAC
1. Construct the circuit on the left.
 2. Open up Simulation Settings, click AC Sweep, fill in (1k:10:10K).
 3. Click the Big Right Arrow to run the simulation.
 4. When the Probe Window appears, click Trace/Add Trace to add V(U6out) and V(u8out) to see the Bode plot.

- To find transient response, use VPULSE
2. Open up Simulation Settings, click AC Sweep, fill in (1k:10:10K).
 3. Click the Big Right Arrow to run the simulation.
 4. When the Probe Window appears, click Trace/Add Trace to add V(U6out) and V(u8out) to see the Bode plot.

Title		
Operational Amplifier		
Size	Document Number	Rev
A4	Chapter 8, Page 1, JCLO	1
Date:	Wednesday, August 24, 2011	Sheet 1 of 1


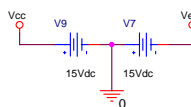


VCC_CIRCLE can be found at GNG/CAPSYM

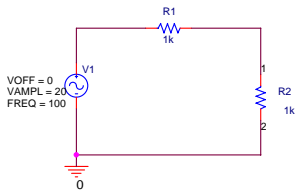


Linear element --- V-I characteristics

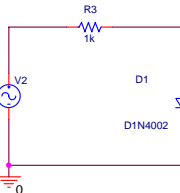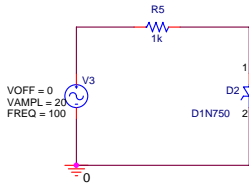1. Construct the circuit on the left.
2. Open up the Simulation Settings, check the Time Domain Transient analysis, and set time period to 10ms.
3. Run the simulation.
4. Click Trace/Add Trace to select I(R2:1). A sine wave is shown.
5. Since time domain t is the default x-axis, we need to change it. Click Plot/Axis Setting/Axis Variables to select x axis =V(R2:1).



Nlinear element --- v-i characteristics

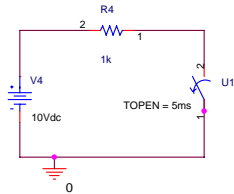
1. Construct the circuit on the left.
2. Open up the Simulation Settings, check the Time Domain Transient analysis, and set time period to 10ms.
3. Run the simulation.
4. Click Trace/Add Trace to select I(D1:1)
5. Since time domain t is the default x-axis, we need to change it. Click Plot/Axis Setting/Axis Variables to select x axis =V(D1:1).
5. Change D to D2, Zener v-i property is obtained.




v-i Characteristics for Thevenin equivalent

1. Construct the circuit on the left.
2. Open up the Simulation Settings, check the Time Domain Transient analysis, and set time period to 10ms.
3. Run the simulation. (it is noted that the switch yields short- and open-circuits)
4. Click Trace/Add Trace to select I(U1:2).
5. Since time domain t is the default x-axis, we need to change it. Click Plot/Axis Setting/Axis Variables to select x axis = V(U1:2).


Title		
BJT		
Size	Document Number	Rev
A4	Chapter 9, page 1	1
Date:	Tuesday, November 08, 2011	Sheet 1 of 1

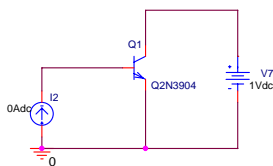

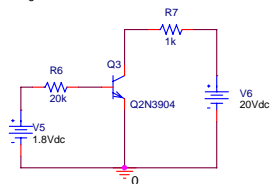
1. To find input characteristic I_b - V_{be} , use DC sweep analysis by open up the Simulation Settings and select primary for current source $I2(=I_b)$ using (0:10u:150u).
2. Run the simulation.
3. Click Trace/Add Trace to find $I_B(Q1)$ for y-axis.
4. Click Plot/Axis Settings/Axis Variable to find $V(Q1:b) - V(Q1:e)$ for x-axis.
5. To find output characteristic I_c - V_{ce} , use dual DC sweep where primary sweep is $V7(=V_{ce})$ using (0:0.01:10) and the second sweep is $I2(=I_b)$ using (0:10u:50u).
6. Click Trace/Add Trace to find $I_C(Q1)$ for y-axis.
7. Click Plot/Axis Settings/Axis Variable to find $V1(V7)$ for x-axis.



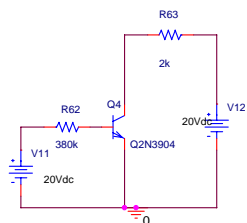
To find input characteristic I_b - V_{be} , use DC sweep on v5 (0:0.01:10)
To find output characteristic I_c - V_{ce} , use dual DC sweep on v6 (0:0.1:10) and V5 (0:0.2:2)



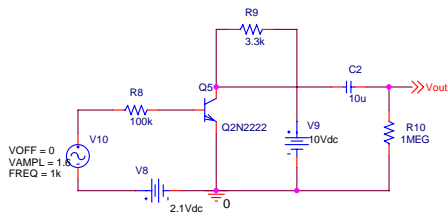To find Q point, simply run bias point analysis and click V and I button.



Title		
BJT		
Size	Document Number	Rev
A4	Chapter 9, Page 2	1
Date:	Wednesday, August 24, 2011	Sheet 2 of 2

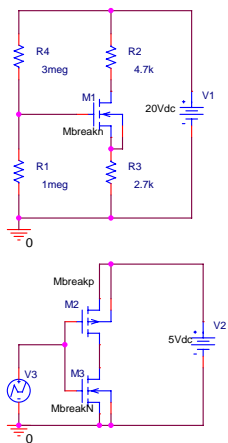

To verify input characteristic:

1. Click Place Part/Breakout/Mbreakn or Mbreakp, drag it to the place you favor. Click the Mbreakn once and from top menu, choose Edit/Model to add/copy the following
 .MODEL Mbreakn NMOS (KP = 50E-6,Vto=2,lambda=0.01)
 .MODEL Mbreakp PMOS (KP = 20E-6,Vto=-2,lambda=0.01)
 to the model editor and then save it.
2. Click twice to edit NMOS, fill in W and L values.
3. Open up the Simulation Settings and select the Primary DC Sweep for V1 (1:1:5).
4. Run the Simulation by click the Big Blue Arrow.
5. When the probe window appears, click Trace/Add Trace and select ID(M1) for y-axis. Click Plot/Axis Setting/Axis Variables and select V(M1,g)-V(M1,s).
6. Click Plot/Label/Line to draw the load line. When drawing, change range of x- and y-axis if necessary.

To verify output characteristic:

1. Open up the Simulation Settings and use DC Dual Sweep. Let Primary Sweep be V2 (1:1:30) and secondarysweep be V1 (1:1:5).
2. Run the simulation.
3. When the probe window appears, click Trace/Add Trace and select ID(M1) for y-axis. Click Plot/AxisSetting/Axis Variables and select V(M1,d)-V(M1,s).
4. Click Plot/Label/Line to draw the load line. When drawing, change range of x- and y-axis if necessary.

DC Bias Point analysis

1. The easiest way is to use Bias Point and then click the icons V and I to find Q point.

CMOS Inverter Gate

1. Construct the circuit on the left.
2. Open up Simulation Setting and choose Time Domain Transient analysis for 5 sec.
3. Run the simulation by clicking the big blue arrow.
4. After the probe window appears, click Trace/Add Trace to select V1(V3) and V(M2:d) for outputs.
5. Adjust range of y-axis for better presentation.

Title		
MOSFET		
Size A4	Document Number Chapter 10, Page 1	Rev 1
Date:	Monday, October 31, 2011	Sheet 1 of 1

Index

- $\Delta - Y$ transform, 84
- n -type material, 233, 309
- p -type material, 233, 309
- pn junction, 233
- 3- dB bandwidth, 213, 218, 223
 - parallel, 219
 - series, 214
- AC excitation, 243
- Admittance, 93
- Amplifiers
 - BJT, 305
 - NMOS, 327
 - op-amp
 - CCCS/current amp, 266
 - CCVS/transresistance amp, 268
 - VCCS/transconductance amp, 267
 - VCVS/voltage amp, 263
- Average value, 89
- Bias circuit, 236, 291
- BJT
 - active region, 289
 - base, 287
 - base bias, 290
 - collector, 287
 - common-base, 305
 - common-collector, 307
 - common-emitter, 303
 - cutoff region, 289
 - emitter, 287
 - emitter follower, 307
 - feedback bias
 - collector-feedback, 297
 - emitter-feedback, 297
 - load line, 291
 - saturation current, 288
 - saturation region, 289
 - self-bias circuit, 297
 - switch, 294
 - thermal voltage, 288
- Bode plot, 201, 210
 - high frequency asymptote, 205
 - line approximation, 203
 - low frequency asymptote, 205
- Bypassing capacitor, 245, 302
- Capacitance, 10, 101, 112, 128, 217
- Characteristic equations, 135, 140, 151, 159, 165, 172, 223
- Circuit analysis, 51
 - loop-current method, 51
 - mesh method, 51
 - node-voltage method, 57
 - nodal method, 57
- Circuit element laws, 8, 91
 - passive
 - Faraday's law, 9
 - generalized Ohm's law, 166
 - Henry's law, 11
 - Ohm's law, 8, 98
- Circuit elements
 - active
 - BJT, 287
 - FET, 317
 - op-amp, 263
 - passive
 - capacitor, 9

- diode, 233
 - inductor, 11
 - resistor, 8
- Circuit network laws
 - KCL, 22
 - KVL, 22
- Circuit quantities
 - charge, 3
 - current, 4
 - energy, 6
 - power, 6
 - voltage, 5
- Circuit theorems
 - equivalence, 37
 - Norton equivalent, 13, 44
 - source transformation, 38, 58
 - Thevenin equivalent, 13, 43, 44, 107
- Clipping, 251
- Complex conjugate, 104, 114
- Conductance, 9, 31
- Continuity of energy, 12
- Conventions
 - current convention, 4
 - passive convention, 5, 8
 - power convention, 6
 - voltage convention, 5
- Current, 4
 - alternating current (AC), 4
 - direct current (DC), 4
- Cutoff frequency, 210
- Deactivation, 65
- Definitions
 - $\alpha = \frac{i_C}{i_E}$, 288
 - $\beta = \frac{i_C}{i_B}$, 288
 - (oc) transresistance gain, 268
 - (oc) voltage gain, 263
 - (sc) current gain, 266
 - (sc) transconductance gain, 267
 - 3-dB bandwidth, 212
 - active elements, 3, 287
 - apparent power, 102
 - branch, 21
 - charge, 4
 - circuit, 21
 - current, 4
 - current gain, 263
 - decade, 202, 207, 215
 - decibels, 201
 - energy, 6
 - ideal diode, 240
 - ideal op-amp/voltage amp, 264
 - impedance, 91
 - linearity, 65
 - loop, 21
 - node, 21
 - octave, 204
 - passive elements, 3
 - phasor, 93
 - pinch-off voltage, 318
 - power, 6
 - RMS (sine function), 89
 - RMS (triangular function), 122
 - voltage, 5
 - Zener diode, 234
- Dependent sources, 14, 45, 49, 57
 - current-controlled current source/CCCS, 15, 300
 - current-controlled voltage source/CCVS, 15
 - voltage-controlled current source/VCCS, 14, 300, 327
 - voltage-controlled voltage source
 - VCVS, 14
 - voltage-controlled voltage source/VCVS, 272
- Depletion
 - pJFET, 320
 - diode, 233
- Diffusion, 233
- Diodes
 - breakdown voltage, 234

- clampers
 - negative, 250
 - negative-biased, 259
 - positive, 250
 - positive-biased, 259
 - clippers
 - negative, 249
 - negative-biased, 259
 - positive, 249
 - positive-biased, 259
 - forward bias, 234
 - full-wave rectifier, 248
 - half-wave rectifier, 247
 - knee/threshold voltage, 234, 237
 - load line, 236
 - piecewise-linear model, 242
 - reverse bias, 234
 - voltage attenuator, 245
- Dynamic equation, 145
- Euler's formula, 90
- Filters
- active
 - Butterworth filter, 277
 - low-pass filter, 277
 - passive, 227
 - band-pass filter, 212
 - band-reject filter, 222
 - high-pass filter, 198
 - low-pass filter, 195
 - notch filter, 220, 222
- Frequencies
- angular frequency, 89
 - break frequency, 199, 205
 - corner frequency, 196, 199, 205
 - cutoff frequency, 199, 205
 - damped frequency, 159, 223
 - half power frequency, 199, 205
 - natural frequency, 159, 218
 - resonant frequency, 212, 218
- Hertz, 90
- Ideal independent sources
- ideal current source, 13
 - ideal voltage source, 12
- Impedance, 93, 166, 214
- Inductance, 11, 99, 128, 217
- JFET
- n*JFET, 317
 - p*JFET, 320
 - depletion region, 318
 - drain, 317
 - gate, 317
 - linear region, 319
 - pinch-off voltage, 318
 - reverse bias, 317
 - saturation region, 319
 - source, 317
 - voltage-controlled resistor, 319
- Laplace transform, 158, 165
- Large-signal analysis
- BJT, 289
 - diodes, 245
 - NMOS, 323
 - PMOS, 323
- Load
- capacitive load, 99
 - inductive load, 99
 - resistive load, 98
- Loading effect, 13, 276
- Logic gates
- BJT
 - NOT, 294
 - CMOS
 - NAND, 332
 - NOR, 332
 - NOT, 332
 - diode
 - AND, 241
 - OR, 257

- Maximum value, 102
- Maximum/peak value, 89
- Mobile carriers
 - electrons, 233, 318
 - holes, 233, 318
- NMOS
 - bias circuit, 323
 - body, 321
 - common-gate, 330
 - common-source, 327
 - cutoff region, 323
 - drain, 321
 - gate, 321
 - large-signal circuit, 324
 - load line, 323
 - saturation region, 323
 - saturation-triode boundary, 323
 - small-signal circuit, 324
 - source, 321
 - source follower, 328
 - switch, 332
 - triode/linear region, 323
- Norton, 44
- Op-amp
 - averaging amp, 272
 - comparator amp, 277
 - difference amp, 274
 - differentiator amp, 280
 - integrator amp, 280, 282
 - inverting amp, 270
 - non-inverting amp, 273
 - summing amp, 272
 - VCVS, 272
 - voltage follower, 276
- Open circuit, 38, 44, 65, 302
- OrCAD, 335
- Permeability, 11
- Permittivity, 10
- Phasor diagram, 95, 104, 105, 217
- Polarity, 5, 321
- Power, 6
 - apparent power, 102
 - average reactive power, 102
 - average real power, 102
 - capacitive power, 99
 - complex power, 102
 - inductive power, 99
 - instantaneous power, 101
 - maximum power transferred, 107
 - power angle, 103
 - power triangle, 103
 - resistive power, 98
 - Volt-Amperes Reactive (VAR), 102
- Power factor
 - lagging power factor, 103
 - leading power factor, 103
- PSpice, 335
 - analyses
 - AC Sweep, 97, 216, 278
 - bias point, 9, 235, 239, 249, 251
 - DC sweep, 9, 235, 239, 249, 251
 - dual DC sweep, 291
 - time domain transient, 11
 - commands
 - PAREMETER, 109
 - plot/axis settings/axis variables, 9, 235, 239, 249, 251
 - plot/label/line, 325
 - plot/label/mark, 9, 235, 239, 249, 251, 325
 - simulation settings, 9, 11, 235, 239, 249, 251
 - trace/add trace, 9, 11, 235, 239, 249, 251
 - trace/cursor, 9, 235, 239, 249, 251
 - edit model
 - NMOS, 332
 - PMOS, 332
 - edit property
 - add new column, 109

- dependent source, 17
- IPRINT, 114
- VPRINT2, 114
- elements
 - C, 11
 - D*, 234
 - D1N4002, 235, 249
 - D1N750, 239
 - D_HI, 278
 - D_LO, 278
 - Do, 234
 - GND, 9
 - L, 12
 - Mbreakn, 324, 325, 332
 - Mbreakp, 324, 332
 - opamp, 265
 - R, 9
 - sD, 234
 - Sw_tClose, 44
 - Sw_tOpen, 44
 - UA471, 265, 278
 - VCC_CIRCLE, 278
- sources
 - E, 14, 272
 - F, 15
 - G, 14
 - H, 15
 - IAC, 13, 97
 - IDC, 9, 13
 - IPWL, 11
 - ISIN, 13, 251
 - VAC, 12, 278
 - VDC, 9, 12
 - VPULSE, 278, 294
 - VPWL, 10, 11, 237
 - VSIN, 12, 251
- Quality factor
 - parallel, 219
 - series, 214
- Quiescent point, 245
- DC operating point, 236, 291, 292, 323
- Resistivity, 8
- Responses
 - forced/steady-state, 127
 - natural/transient, 127
- RMS/Effective value, 89
- Root Means Square value (RMS), 102
- Roots
 - second-order system, 159
- Sallen-Key topology, 277
- Saturation, 251
- Schockley equation, 234
- Second-order systems, 157
 - parallel, 158
 - series, 164
- Selective networks, 195, 213
- Short circuit, 39, 44, 65, 302
- Signals
 - complex, 89
 - exponential, 89
 - sinusoidal, 90
- Small-signal analysis
 - BJT, 299
 - diodes, 245
 - NMOS, 326
- Steady-state error, 142
- Summing-point constraint, 264
- Supermesh, 22, 25, 55
- Supernode, 23, 25, 63, 314
- Superposition, 65, 245, 274
- Systems
 - first-order systems, 130, 155, 157
 - forced systems, 157
 - second-order systems, 157, 278
 - unforced systems, 157
- Thermal voltage, 234
- Thevenin, 43, 108, 177, 236, 271, 295
- Time constant, 132, 135
- Time line, 129

Transfer function, 196, 236, 249

Transient responses

critically damped response, 160, 166

first-order systems, 130

overdamped response, 159, 166

second-order systems, 157

underdamped response, 160, 166

Transistors

bipolar

*n*pn BJT, 287

*p*np BJT, 287, 309

unipolar

*n*JFET, 317

*p*JFET, 317

IGFET/MOSFET, 317

NMOS, 317

PMOS, 317

Virtual open circuit, 264

Virtual short circuit, 264

Wheatstone bridge, 64, 275

Zener

voltage regulator, 237

Bibliography

- [1] A. R. Hambley, *Electrical Engineering, Principles and Applications, third Edition*. Prentice Hall, 2005.
- [2] C. R. Paul, *Fundamentals of Electric Circuits Analysis*. Wiley, 2001.
- [3] J. W. Nilsson, *Electric Circuits*. Addison Wesley, 1984.
- [4] P. Z. Peebles and T. A. Giuma, *Principles of Electrical Engineering*. McGraw Hill, 1991.
- [5] J. Clemons, F. Kerr, F. Evangelisti and C. Klingensmith *Introductory Electronic Devices and Circuits*. Prentice Hall, 1994.
- [6] <http://www.ee.cyu.edu.tw/garylee/pspice/animation/index.htm>
- [7] <http://www.seas.upenn.edu/~jan/spice/PSPicePrimer.pdf>
- [8] <http://www.electronics-lab.com/downloads/schematic/013/tutorial/PSPICE.pdf>
- [9] <http://people.msoe.edu/~saadat/pspiceintro253.htm>
- [10] <http://www1bpt.bridgeport.edu/~thapa/eleg458/tut/pspice/PSPICE.MOS.TUT5.pdf>
- [11] http://www.ee.nmt.edu/~rison/ee321_fall02/Tutorial.html



書名: **eThinking in Circuits with PSpice©**
ISBN 978-957-41-8721-8
著作人: 羅吉昌
封面設計: 羅吉昌
著作完成日: 西元2011年10月31日



著作人資訊:
出版者: 羅吉昌

印製者: 淵明印刷有限公司
地址: 台北縣永和市福和路164號4樓
網址: <http://www.ym.com.tw/>
電話: 02-89255555

出版日期: 西元2012年01月

本書受著作權法保護；未經作者同意，翻印，翻譯必究




Date

Dept.

Institution

Name

$$G(s) = \frac{50}{s(s+3)(s+6)}$$

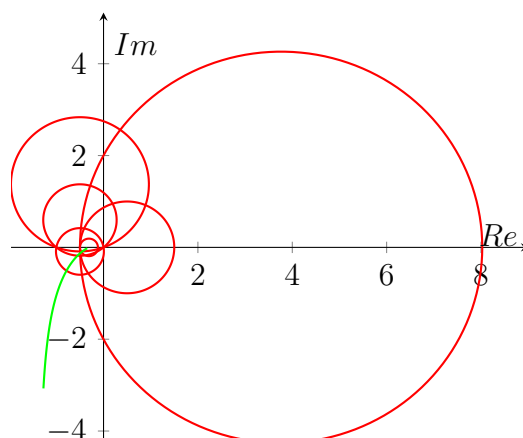

About the author

J.C. LO is a Professor of Mechanical Engineering at National Central University, Taiwan, receiving his Ph.D. degree in Electrical Engineering from Michigan State University, East Lansing, Michigan, in 1990. Since graduation, he joined the Mechanical Engineering, actively teaching in circuits, microprocessor, and automatic control and deeply indulging in the area of fuzzy, robust, linear and nonlinear control.

He has served as a regular peer reviewer for many renowned technical Journals and Institutions, domestic and abroad. His current interests focus on homogenously polynomial parameter dependent Lyapunov methods analyzing stability/stabilization problems via Linear Matrix Inequalities and Sum of Squares, with publication credits for numerous papers and reports in his area of expertise.

ISBN 978-957-41-8721-8



National Central University <http://www.ncu.edu.tw> Cover Illustration by J.C. LO