

Chapter 3

DC Circuits

eThinking in Circuits with PSpice

Mechanical Engineering
National Central University

March 12, 2017

Outlines



1 Circuit Theorems

- Equivalence
- Source transformations
- Circuit reductions
- Thevenin/Norton Equivalents

2 Circuits Analysis

- Loop-current/Mesh method
- Node-voltage method

3 Superposition

- Independent sources
- Dependent sources



Equivalence

Two electrical circuits are equivalent if they have the same $v-i$ characteristics at the external terminals,

$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.



Equivalence

Two electrical circuits are equivalent if they have the same $v - i$ characteristics at the external terminals,

$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.

For R_1 , $I_{R_1}^A = I_{R_1}^B$, $V_{R_1}^A = V_{R_1}^B$, $v-i$ are the same

Equivalence

Two electrical circuits are equivalent if they have the same $v - i$ characteristics at the external terminals,

$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.

For R_1 , $I_{R_1}^A = I_{R_1}^B$, $V_{R_1}^A = V_{R_1}^B$, v-i are the same

For R_2 , $I_{R_2}^A = I_{R_2}^B$, $V_{R_2}^A = V_{R_2}^B$, v-i are the same

Equivalence

Two electrical circuits are equivalent if they have the same $v - i$ characteristics at the external terminals,

$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.

For R_1 , $I_{R_1}^A = I_{R_1}^B$, $V_{R_1}^A = V_{R_1}^B$, v-i are the same



For R_2 , $I_{R_2}^A = I_{R_2}^B$, $V_{R_2}^A = V_{R_2}^B$, v-i are the same

\vdots

Equivalence

Two electrical circuits are equivalent if they have the same $v - i$ characteristics at the external terminals,

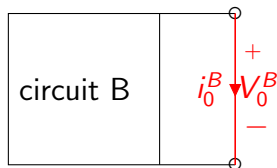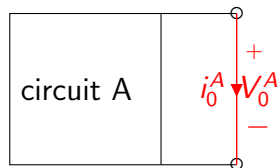$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.

For R_1 , $I_{R_1}^A = I_{R_1}^B$, $V_{R_1}^A = V_{R_1}^B$, v-i are the same

For R_2 , $I_{R_2}^A = I_{R_2}^B$, $V_{R_2}^A = V_{R_2}^B$, v-i are the same

⋮

including $R = 0$ and $R = \infty$, v-i are the same

Equivalence

Two electrical circuits are equivalent if they have the same $v - i$ characteristics at the external terminals,

$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.

For R_1 , $I_{R_1}^A = I_{R_1}^B$, $V_{R_1}^A = V_{R_1}^B$, $v-i$ are the same

For R_2 , $I_{R_2}^A = I_{R_2}^B$, $V_{R_2}^A = V_{R_2}^B$, $v-i$ are the same



\vdots

including $R = 0$ and $R = \infty$, $v-i$ are the same

Equivalence

Two electrical circuits are equivalent if they have the same $v - i$ characteristics at the external terminals,

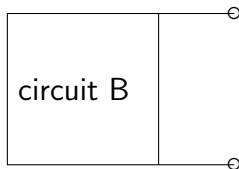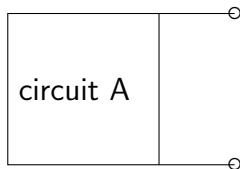$\forall R$, including $R = 0$ and $R = \infty$.



Circuits A and B are different in structure, but from the terminal.

For R_1 , $I_{R_1}^A = I_{R_1}^B$, $V_{R_1}^A = V_{R_1}^B$, v-i are the same

For R_2 , $I_{R_2}^A = I_{R_2}^B$, $V_{R_2}^A = V_{R_2}^B$, v-i are the same



\vdots

including $R = 0$ and $R = \infty$, v-i are the same


Simply put it,

Telling no difference seen from v-i, at the output terminal.


Thevenin & Norton

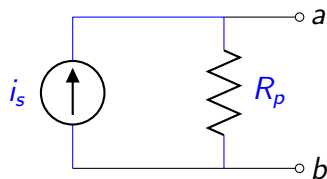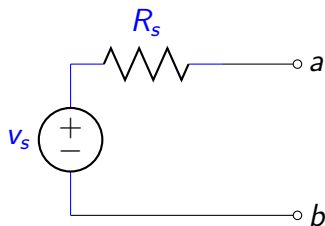

Thevenin & Norton

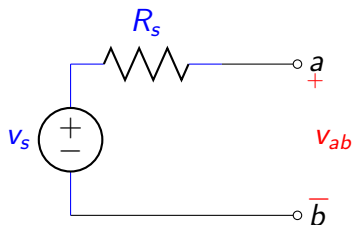


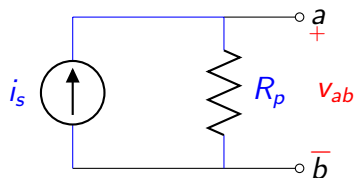Open circuit ($R = \infty$) : $v_{ab} = v_s$




Open circuit : $v_{ab} = i_s R_p$

Thevenin & Norton

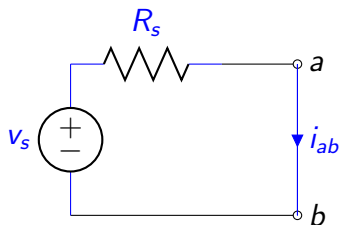

Open circuit ($R = \infty$) : $v_{ab} = v_s$

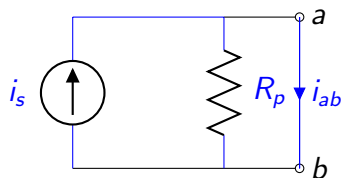
Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$



Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$


Thevenin & Norton

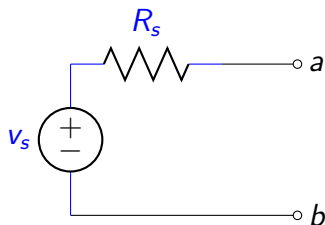

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$

Due to Equivalence: $v_s = i_s R_p$,


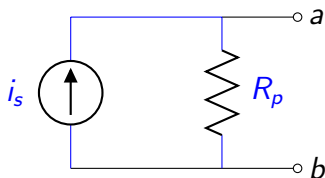


Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$

$\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Thevenin & Norton

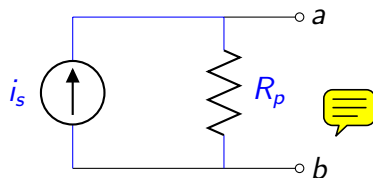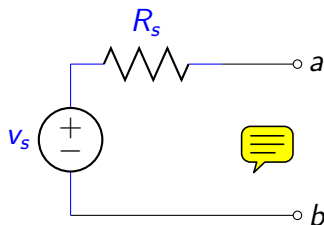

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$



Due to Equivalence: $v_s = i_s R_p$, $\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Can you now transform between these two sources?

Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$

Thevenin & Norton

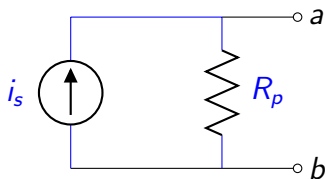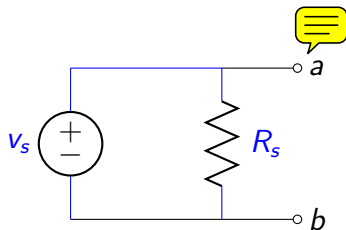

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$



Due to Equivalence: $v_s = i_s R_p$, $\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Can you now transform between these two sources?

Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$

Thevenin & Norton

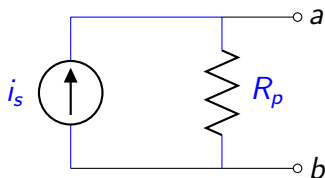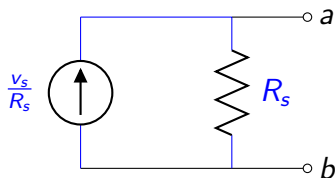

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$



Due to Equivalence: $v_s = i_s R_p$, $\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Can you now transform between these two sources?

Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$

Thevenin & Norton

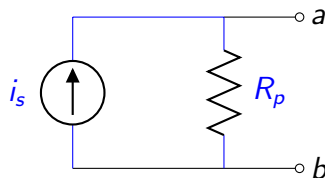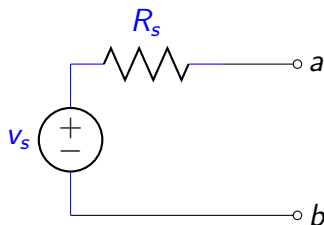

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$



Due to Equivalence: $v_s = i_s R_p$, $\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Can you now transform between these two sources?

Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$

Thevenin & Norton

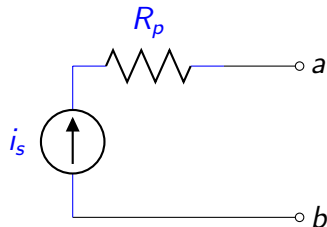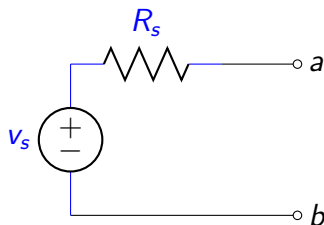

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$



Due to Equivalence: $v_s = i_s R_p$, $\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Can you now transform between these two sources?

Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$

Thevenin & Norton

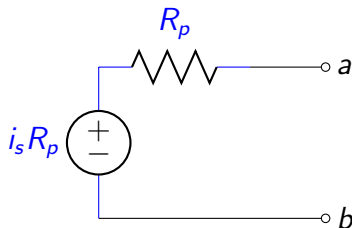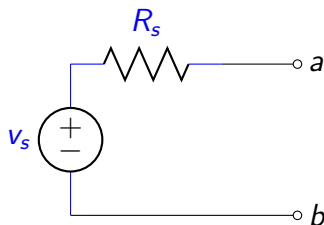

Open circuit ($R = \infty$) : $v_{ab} = v_s$

Short circuit ($R = 0$) : $i_{ab} = \frac{v_s}{R_s}$


Due to Equivalence: $v_s = i_s R_p$, $\frac{v_s}{R_s} = i_s$, $R_s = R_p$

Can you now transform between these two sources?

Open circuit : $v_{ab} = i_s R_p$

Short circuit: $i_{ab} = i_s$


Series

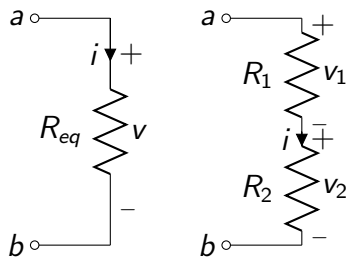

By equivalence

$$R_{eq} = R_1 + R_2$$


Series

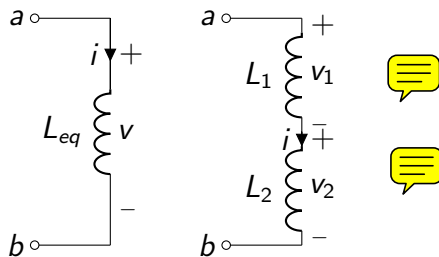

By equivalence

$$L_{eq} = L_1 + L_2$$

Series


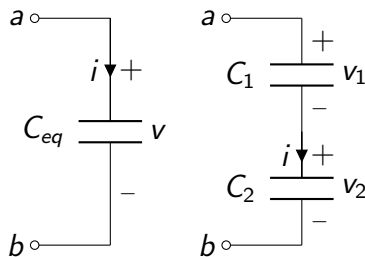


By equivalence

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



Parallel

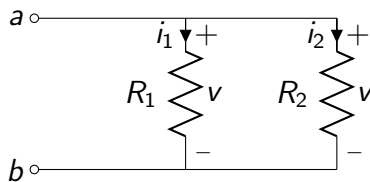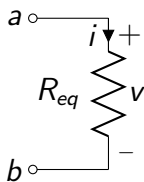


By equivalence

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$




Parallel

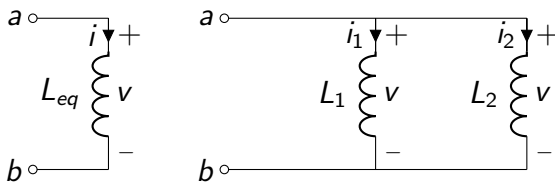

By equivalence

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

Parallel


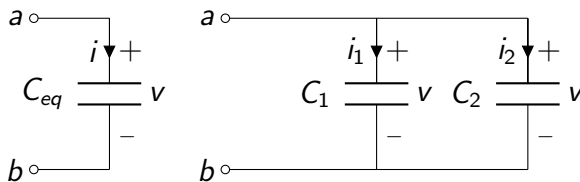


By equivalence


$$C_{eq} = C_1 + C_2$$



Thevenin equivalent

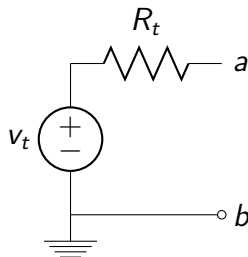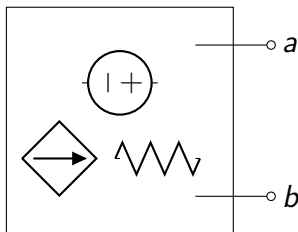


Thevenin equivalent

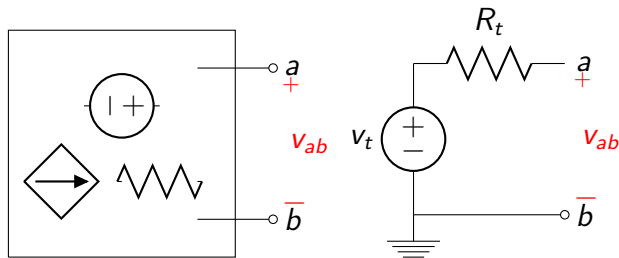

Open circuit ($R = \infty$) : $V_{ab} = V_t = V_{oc}$

Thevenin equivalent

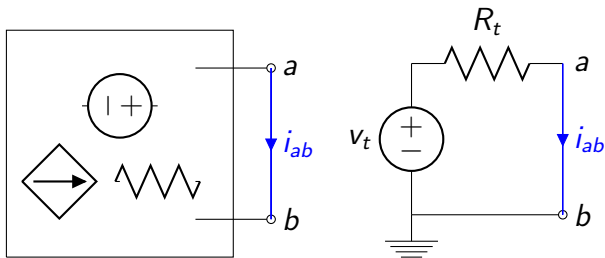


Open circuit ($R = \infty$) : $V_{ab} = V_t = V_{oc}$

Short circuit ($R = 0$) : $i_{ab} = \frac{V_t}{R_t} = i_{sc}$



Thevenin equivalent

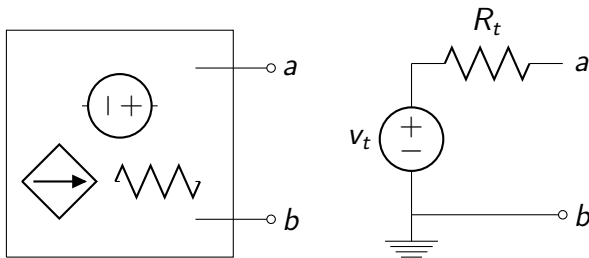


Open circuit ($R = \infty$) : $V_{ab} = V_t = V_{oc}$

Short circuit ($R = 0$) : $i_{ab} = \frac{V_t}{R_t} = i_{sc}$

We need to solve the circuit on the left or use measurement.

Thevenin equivalent

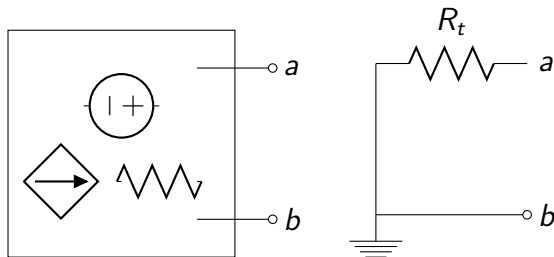



Open circuit ($R = \infty$) : $V_{ab} = V_t = V_{oc}$

Short circuit ($R = 0$) : $i_{ab} = \frac{V_t}{R_t} = i_{sc}$


We need to solve the circuit on the left or use measurement.

A quick way to find R_t is setting v_t to zero.

Norton equivalent

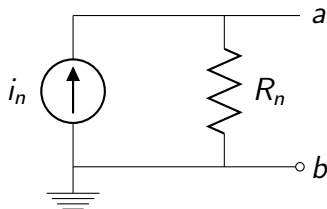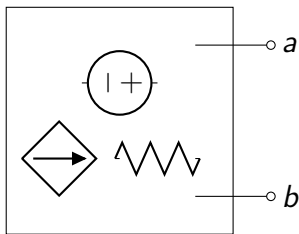


Norton equivalent

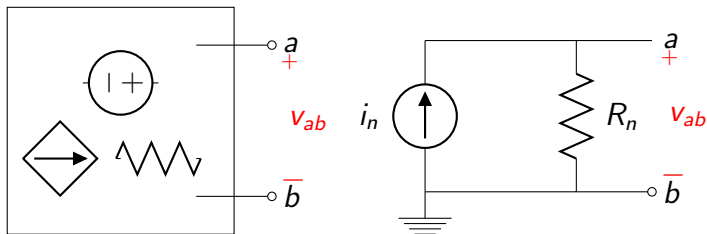

Open circuit ($R = \infty$) : $v_{ab} = i_n R_n = i_s R_n = \underline{v_{oc}}$


Norton equivalent

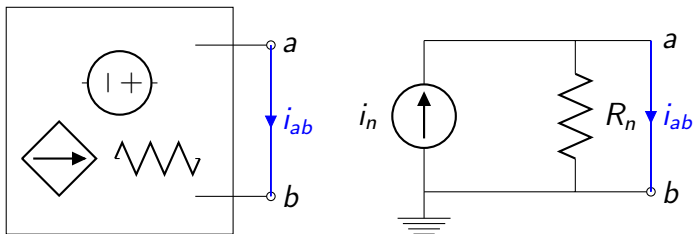

Open circuit ($R = \infty$) : $v_{ab} = i_n R_n = i_s R_n = v_{oc}$

Short circuit ($R = 0$) : $i_{ab} = i_n = i_{sc}$

Norton equivalent


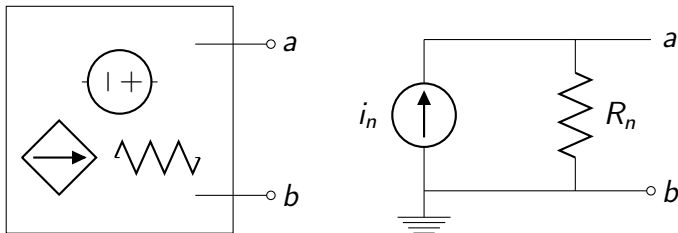


Open circuit ($R = \infty$) $v_{ab} = i_n R_n = i_s R_n = v_{oc}$

Short circuit ($R = 0$) $i_{ab} = i_n = i_{sc}$

We need to solve the circuit on the left or use measurement

Norton equivalent

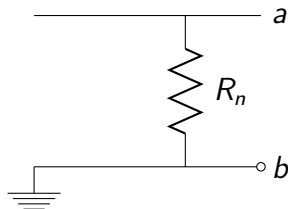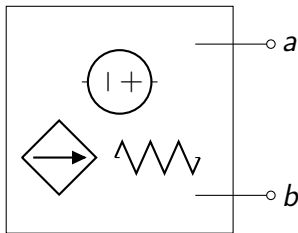


Open circuit ($R = \infty$) : $v_{ab} = i_n R_n = i_s R_n = v_{oc}$

Short circuit ($R = 0$) : $i_{ab} = i_n = i_{sc}$

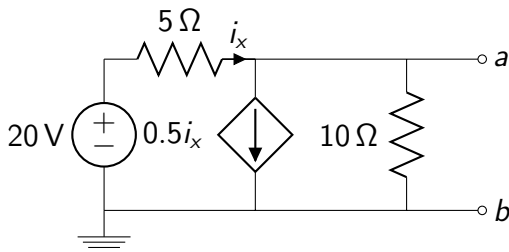We need to solve the circuit on the left or use measurement
A quick way to find R_t is setting i_n to zero.





$$(a) \ i = 0.5i + \frac{1}{10}, \quad i = 0.2A, \quad R_t = \frac{1}{0.2} = 5\Omega.$$


(b) Open circuit

$$\frac{20 - V_a}{5} = 0.5i_x + \frac{V_a}{10}$$

$$\frac{V_a}{10} = i_x - 0.5i_x.$$

Solving, we have $i_x = 2A$. Thus $V_a = 10V = V_{oc}$.
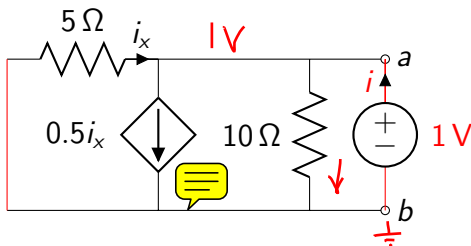
$$(c) \text{ Short Circuit: } i_x = \frac{20}{5} = 4A, \quad i_{sc} = 2A.$$




(a) $i_x = 0.5i_x + \frac{1}{10}$, $i_x = 0.2A$, $R_t = \frac{1}{0.2} = 5\Omega$.
 (b) Open circuit

$$\frac{20 - V_a}{5} = 0.5i_x + \frac{V_a}{10}$$

$$\frac{V_a}{10} = i_x - 0.5i_x.$$

Solving, we have $i_x = 2A$. Thus $V_a = 10V = V_{oc}$.

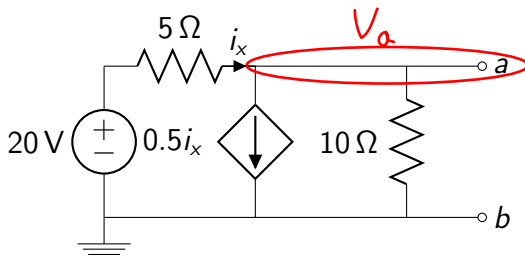(c) Short Circuit: $i_x = \frac{20}{5} = 4A$, $i_{sc} = 2A$.



(a) $i = 0.5i + \frac{1}{10}$, $i = 0.2A$, $R_t = \frac{1}{0.2} = 5\Omega$.

(b) Open circuit




$$\frac{20 - V_a}{5} = 0.5i_x + \frac{V_a}{10}$$

$$\frac{V_a}{10} = i_x - 0.5i_x$$



Solving, we have $i_x = 2A$. Thus $V_a = 10V = V_{oc}$.

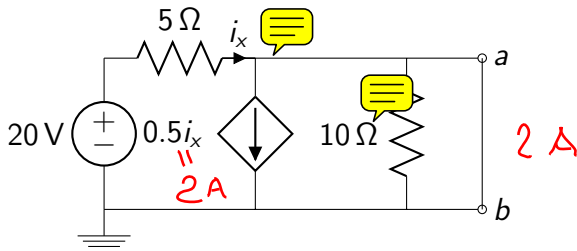(c) Short Circuit: $i_x = \frac{20}{5} = 4A$, $i_{sc} = 2A$.



(a) $i = 0.5i + \frac{1}{10}$, $i = 0.2A$, $R_t = \frac{1}{0.2} = 5\Omega$.

(b) Open circuit

$$\frac{20 - V_a}{5} = 0.5i_x + \frac{V_a}{10}$$

$$\frac{V_a}{10} = i_x - 0.5i_x.$$


Solving, we have $i_x = 2A$. Thus $V_a = 10V = V_{oc}$.

(c) Short Circuit: $i_x = \frac{20}{5} = 4A$, $i_{sc} = 2A$.



- ① Loop-current method: Adding voltage
 - ▶ Only voltage sources
 - ▶ Involve current sources
- ② Node-voltage method: Adding current
 - ▶ Only current sources
 - ▶ Involve voltage sources

Example 3.8

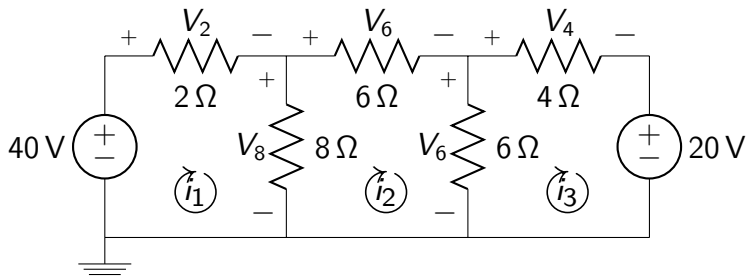


$$-40 + 2i_1 + 8(i_1 - i_2) = 0$$

$$-[-8(i_2 - i_1)] + 6i_2 + 6(i_2 - i_3) = 0$$

$$-[-6(i_3 - i_2)] + 4i_3 + 20 = 0$$

Example 3.8

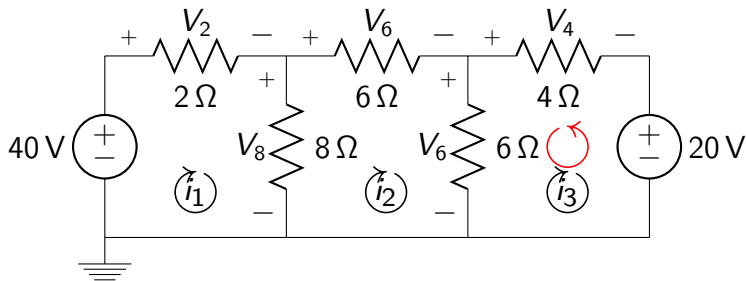

$$-40 + 2i_1 + 8(i_1 - i_2) = 0$$


$$-[-8(i_2 - i_1)] + 6i_2 + 6(i_2 - i_3) = 0$$

$$-[-8(i_2 - i_1)] + 6i_2 + 6(i_2 + i_3) = 0$$

$$-[-6(i_3 - i_2)] + 4i_3 + 20 = 0$$

$$6(i_3 + i_2) - [-4i_3] - 20 = 0$$

Example 3.8

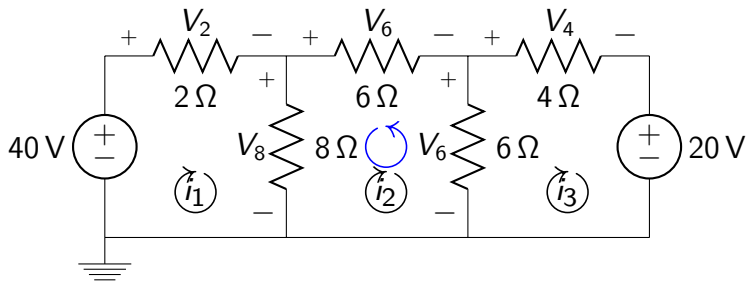

$$-40 + 2i_1 + 8(i_1 - i_2) = 0$$


$$-[-8(i_2 - i_1)] + 6i_2 + 6(i_2 - i_3) = 0$$

$$8(i_2 + i_1) - [-6i_2] - [-6(i_2 + i_3)] = 0$$

$$-[-6(i_3 - i_2)] + 4i_3 + 20 = 0$$

$$-[-6(i_2 + i_3)] + 4i_3 + 20 = 0$$

Example 3.16

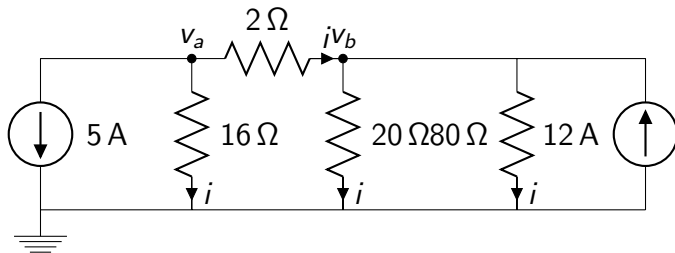

Assign leaving current to be positive

$$5 + \frac{v_a}{16} + \frac{v_a - v_b}{2} = 0$$

$$\frac{v_b}{20} + \frac{v_b}{80} - \frac{v_a - v_b}{2} - 12 = 0$$

Solving, we have $v_a = 48V$, $v_b = 64V$.

Linear system

$$f(ax_1 + bx_2) = af(x_1) + bf(x_2), a, b \in R.$$

Total response = sum of individual responses




Independent voltage source \rightarrow a short circuit





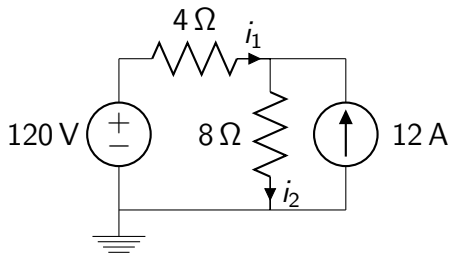
Independent current source \rightarrow an open circuit







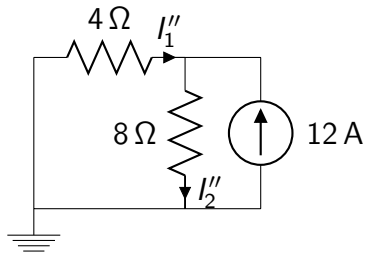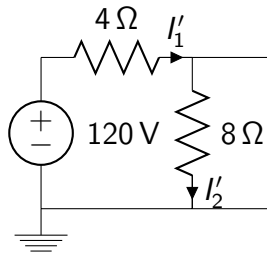
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$




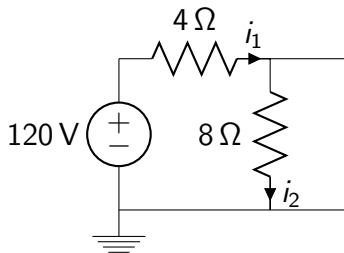


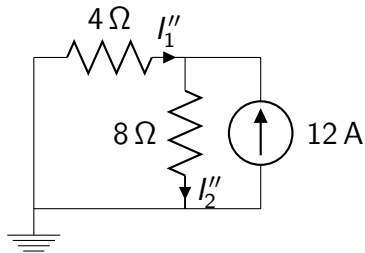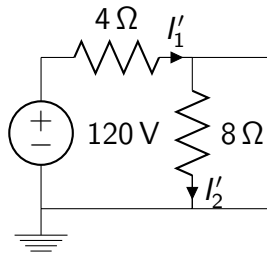
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$




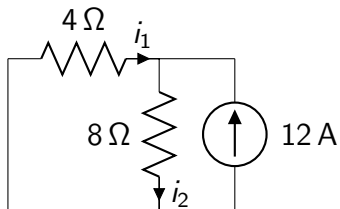


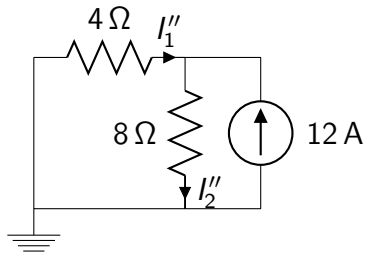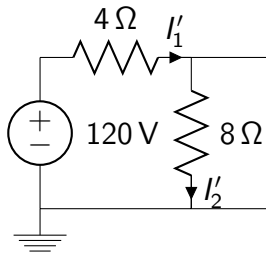
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$




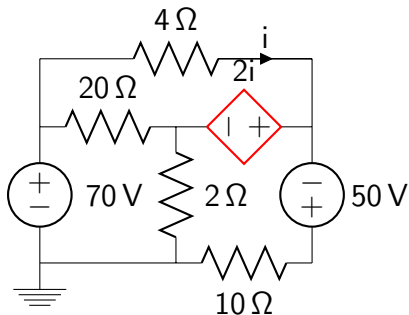


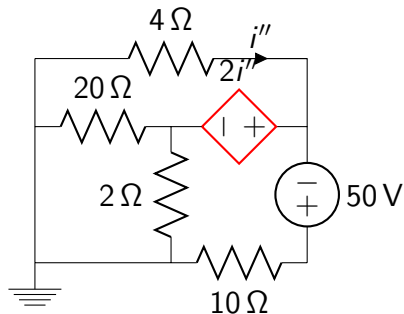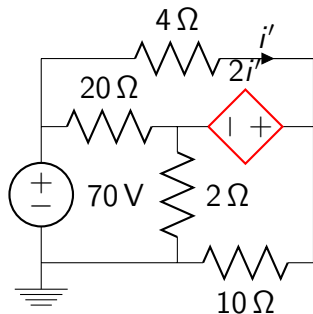
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$




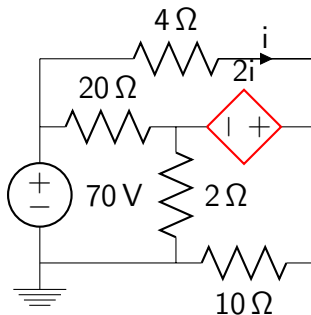


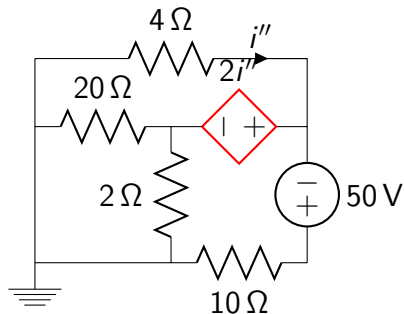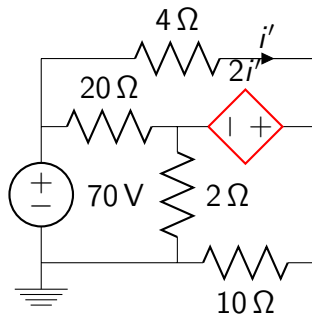
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$



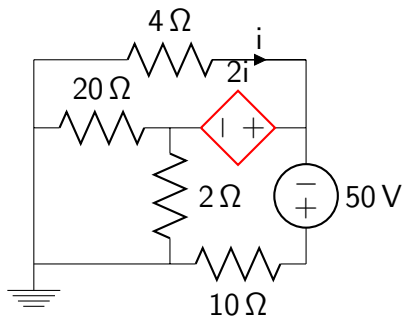


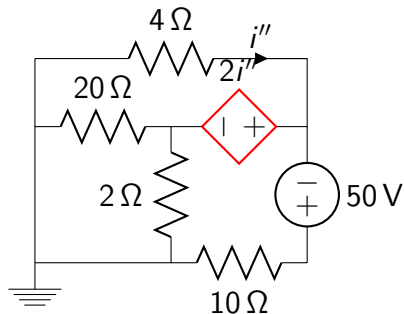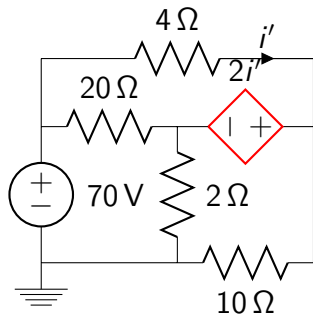
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$



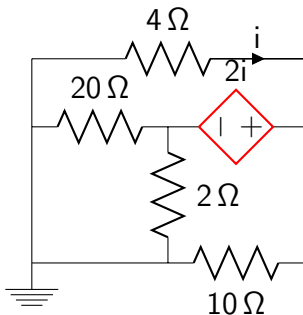
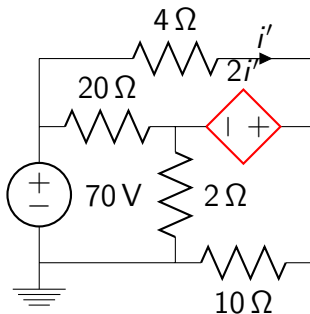
$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$



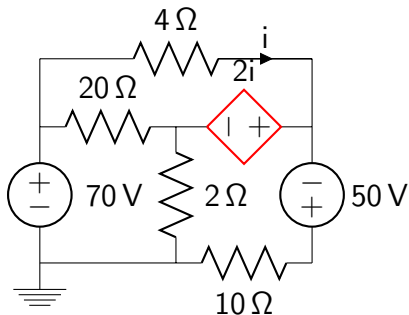

No need to disable the dependent source.

$$i_1 = i'_1 + i''_1 \quad i_2 = i'_2 + i''_2$$

